



# Electronics Switches & Controls

---

- **Conventional controls**
  - **Potentiometer**
  - **switches**
- **Transistor as switches and controls**
  - **FET-based**
  - **BJT-based**
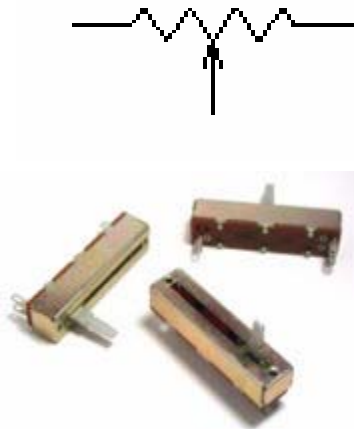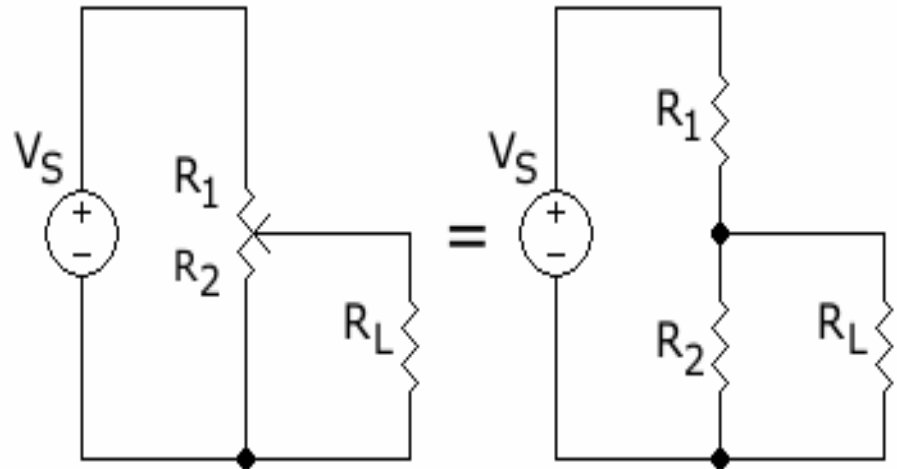
# Variable potentiometers

- Variable resistance sometime needed (see Labs)
- potentiometer provides such a variable resistance.
- Make sure the circuit works for any transistor from this batch.



$$V_L = \frac{R_2 R_L}{R_1 R_L + R_2 R_L + R_1 R_2} \cdot V_s$$

# Electronics Switches

---


**-Switches are elements with two states « Open » and « Close »**



SPST : Single Pole Single Throw



SPDT : Single Pole Double Throw

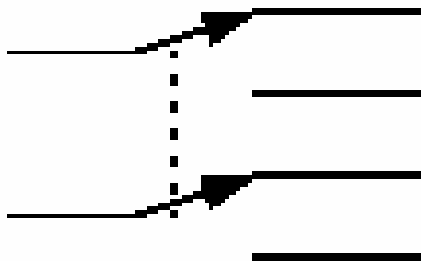


DPST : Double Pole Double Throw

**-Simplest switches are mechanical switches**


# Refresher on transistors

-Transistors can be used as switches, to control resistance, etc...

## ■BJT

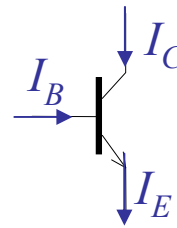


NPN

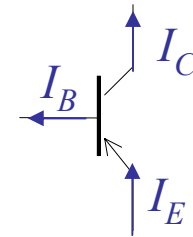


PNP

$$\rightarrow I_E = I_B + I_C$$

## ■FET

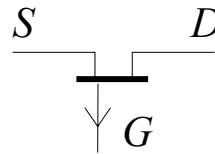

JFET P-channel

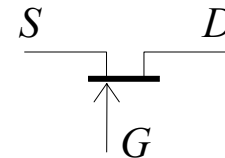


JFET N-channel


$$\rightarrow I_G = I_S + I_D$$

# Operating mode a a NPN BJT


<b>Active mode :</b>	$V_{BE} \approx 0.7V$	$\sim 0.3V < V_{CE} < V_{CC}$	$I_c \approx \beta I_B$
<b>Open mode :</b>	$I_B \cong 0$	$V_{CE} \cong V_{CC}$	$I_C \approx 0$
<b>Sat. mode :</b>	$V_{BE} \approx 0.8V$	$V_{CE} \approx 0.2V$	$I_c \neq \beta I_B$

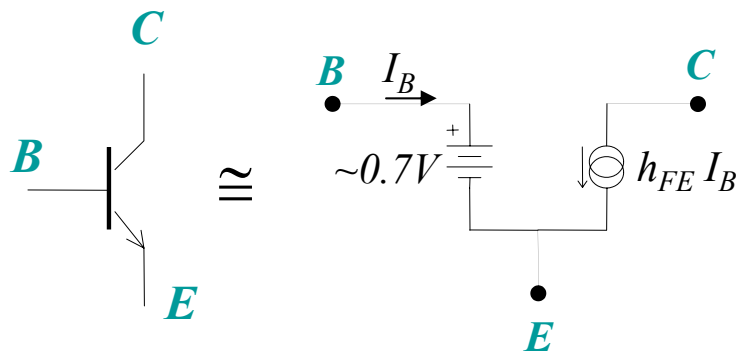

*Active mode*

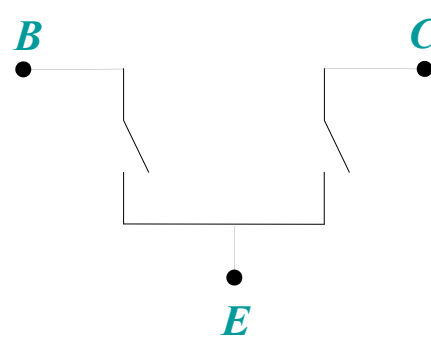

*Open mode*

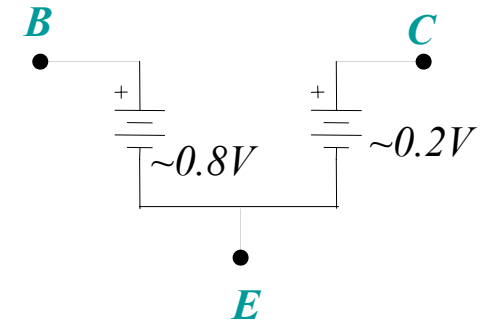


*Saturated mode*


$V_{CC}$  = external voltage source supplyin C et E.  $V_{CE}$  cannot be larger than  $V_{CC}$ !

# Operating mode a a NPN BJT


<b>Active mode:</b>	$V_{BE} \approx -0.7V$	$\sim -0.3V < V_{CE} < V_{CC}$	$(< 0)$	$I_c \approx \beta I_B$
<b>Open mode:</b>	$I_B \cong 0$	$V_{CE} \cong V_{CC}$		$I_C \approx 0$
<b>Sat. Mode:</b>	$V_{BE} \approx -0.8V$	$V_{CE} \approx -0.2V$		$I_c \neq \beta I_B$

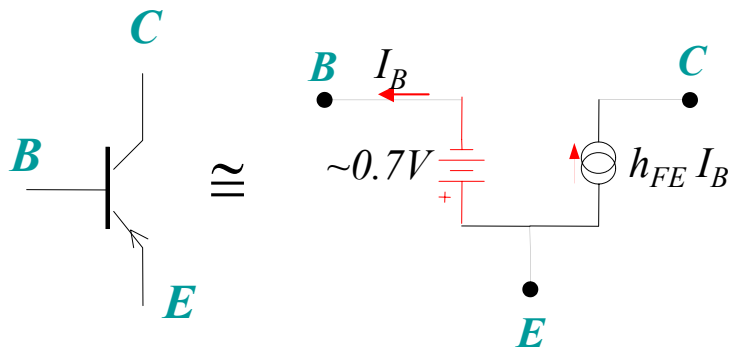

Active mode

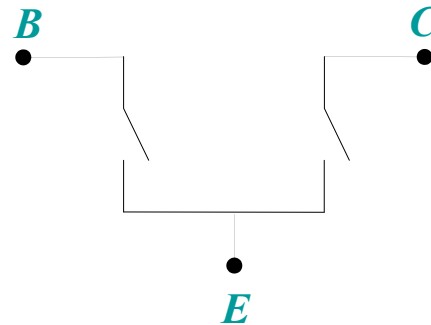


Open mode

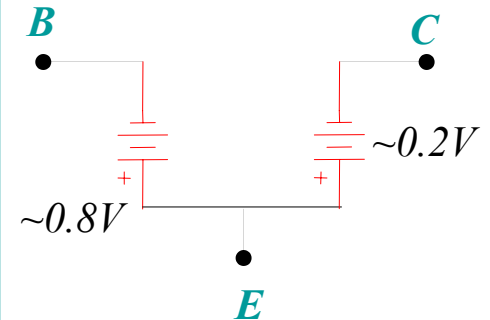


Saturated mode


# BJT as a switch

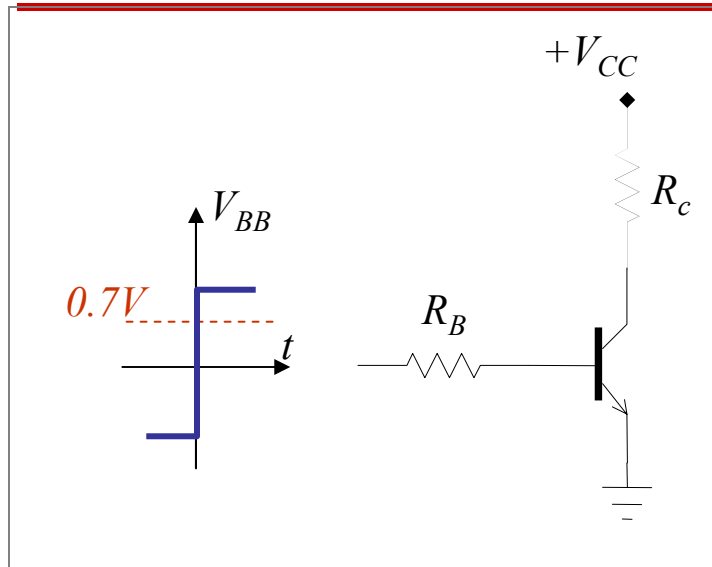

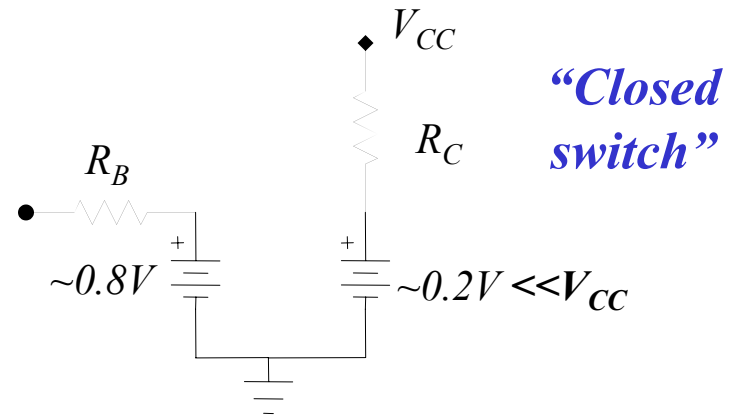$t > 0$  :  $V_{BE} > \sim 0.8V$ , so that  $R_C I_C \sim V_{CC}$   
 $\rightarrow V_{CE} \sim \text{few } 100mV$





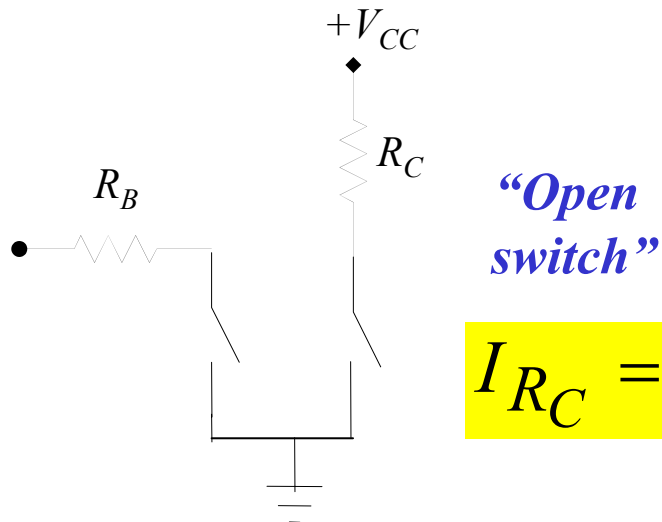
$t < 0$  :  $V_{BE} < 0.7V \rightarrow$  Open mode



$$I_{R_C} = 0$$

$$I_{R_C} = \frac{V_{CC} - 0.2}{R_C} \cong \frac{V_{CC}}{R_C}$$

# BJT as a switch

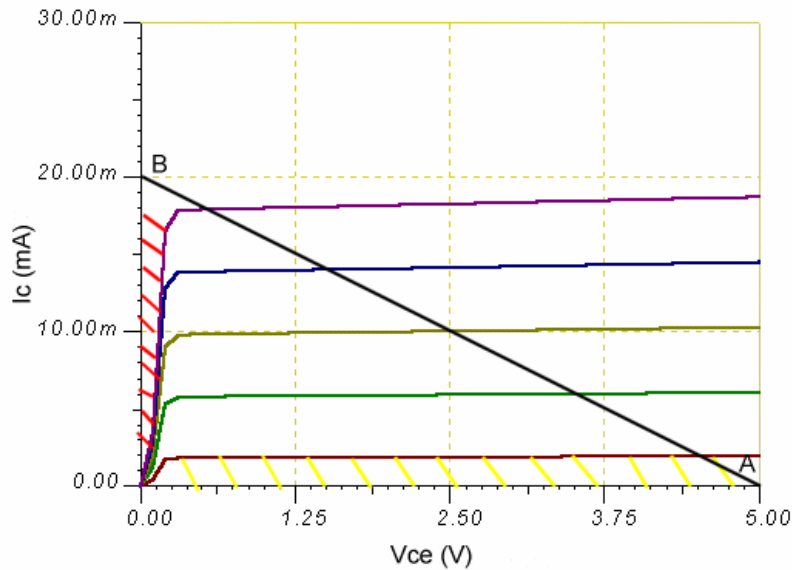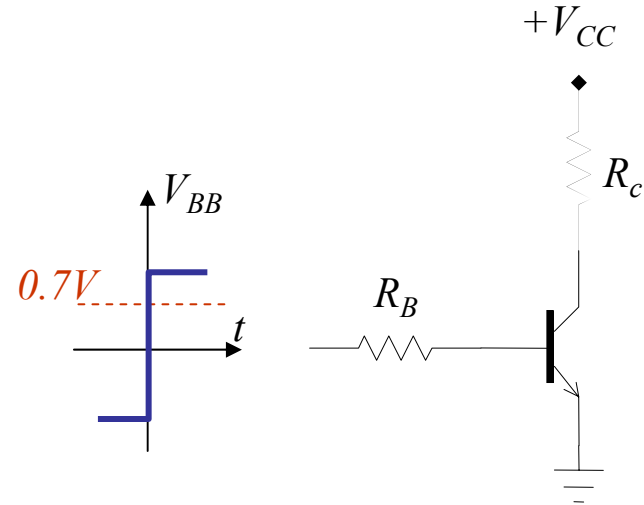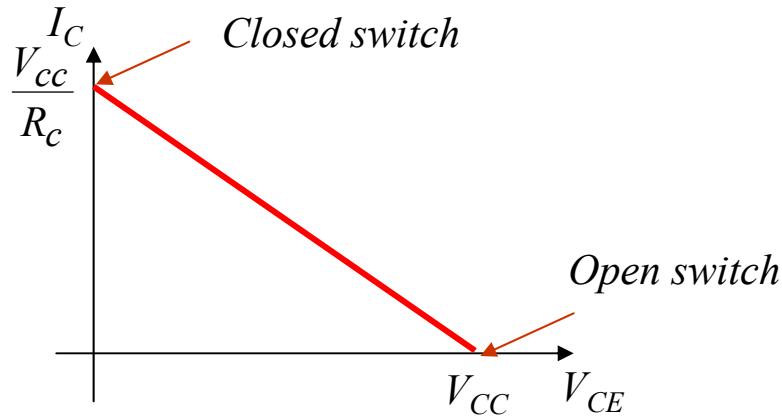


$$I_{B_{\min}} \text{ (Closed switch)} \cong \frac{V_{cc}}{R_c \beta} \cong \frac{V_{BE_{\min}} - 0.8}{R_B}$$


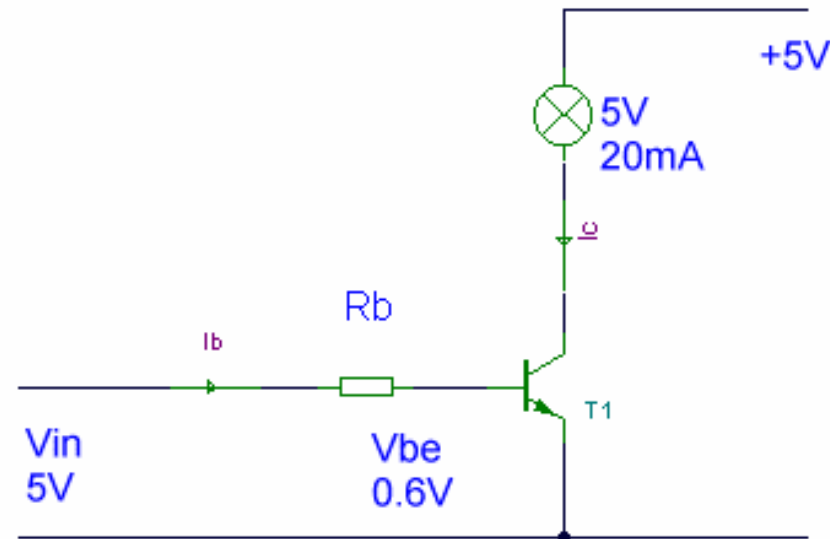
# BJT as a switch: turning on/off a light


- BJT with 5 V voltage source,
- Design a system to switch a 20 mA, 5V lamp on and off,
- The gain factor for a given batch of transistor varies between  $100 < \beta < 500$ ,
- Make sure the circuit works for any transistor from this batch.



$$i_B = \frac{1}{\beta} i_c \Rightarrow \max(i_B) = \frac{1}{\min(\beta)} i_c \Rightarrow \max(i_B) = 0.2 \text{ mA}$$

$$V_{IN} = V_{BE} + R_B i_B \Rightarrow R_B = \frac{V_{IN} - V_{BE}}{i_B} = \frac{5 - 0.6}{0.2} 10^3 = 22 \text{ k}\Omega$$

# BJT as an amplifier

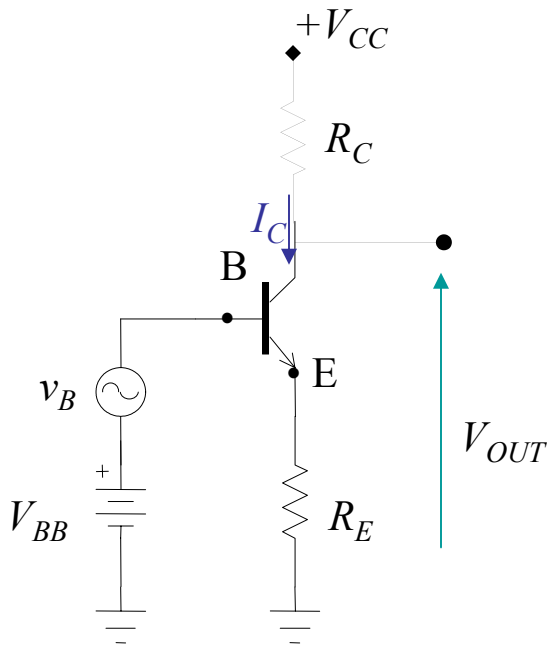

*assumptions :*

- Transistor operates in **active mode** when  $v_B = 0$
- **Amplitude** of  $v_B$  signal **small** enough to have active mode operation

● In 1<sup>st</sup> approximation :  $V_B \equiv V_{BB} + v_b$

$$\rightarrow I_E \approx \frac{V_B - V_{BE}}{R_E} \approx I_C = \bar{I}_C + i_c \quad (I_B \ll I_C)$$

*Neglecting variation of  $V_{BE}$  :*  $\rightarrow i_c \approx \frac{v_B}{R_E}$

Finally :  $V_{out} = V_{cc} - R_C I_C = V_S + v_s$  with :  $V_S = V_{cc} - R \cdot \bar{I}_C$

and


$$v_s = -R_C i_c = -\frac{R_C}{R_E} v_b$$

Signal  $v_B$  is amplified by a factor

$$A_v = -\frac{R_C}{R_E}$$
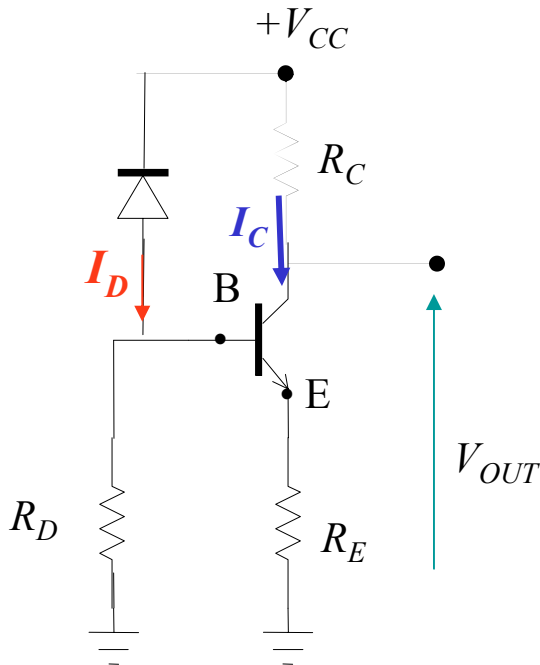
# BJT as an amplifier: light detection

- Previous circuit can be used to amplify low intensity signal, e.g. such as produced in photodiode (typically  $1\text{ }\mu\text{A}/1\text{ }\mu\text{W}$  of incident light)
- Circuit is modified as follows:



*Output voltage is given by:*

$$V_{OUT} = V_{CC} - R_C I_C$$

*From ground-E-B-ground loop:*


$$I_C = \frac{V_B - V_{BE}}{R_E} \approx \frac{R_D I_D - V_{BE}}{R_E} \approx \frac{R_D I_D - 0.7}{R_E}$$

*Finally output voltage is:*

$$\begin{aligned} V_{OUT} &= V_{CC} - (R_D I_D - 0.7) \frac{R_C}{R_E} \\ &= V_{CC} + 0.7 \frac{R_C}{R_E} - \frac{R_D R_C}{R_E} I_D \\ &= \bar{V}_{OUT} - \frac{R_D R_C}{R_E} I_D \end{aligned}$$
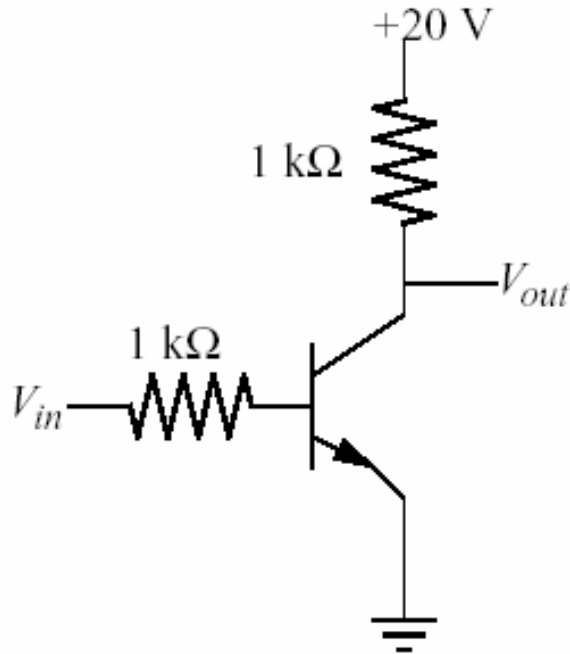
# Two-states electronics

■ When  $V_{in}=0$  transistor is open,  $V_{out} = 20 \text{ V}$




■ As  $V_{in}$  increases the transistor turns on (active mode) and current begins to flow  $\rightarrow V_{out}$  is lowered toward ground.

■ Eventually  $V_{BE} \sim 0.8 \text{ V}$  (saturated mode), and when  $V_{in} \sim 1 \text{ V}$   
 $\rightarrow I_c = \beta I_b \sim 20 \text{ mA}$  so  $V_{OUT}$  is close to 0

■ This circuit has only two output states (with exception of  $0.8 \text{ V} < V_{in} < 1 \text{ V}$ )

■ Two-states electronics important components of digital electronics

# FET as control

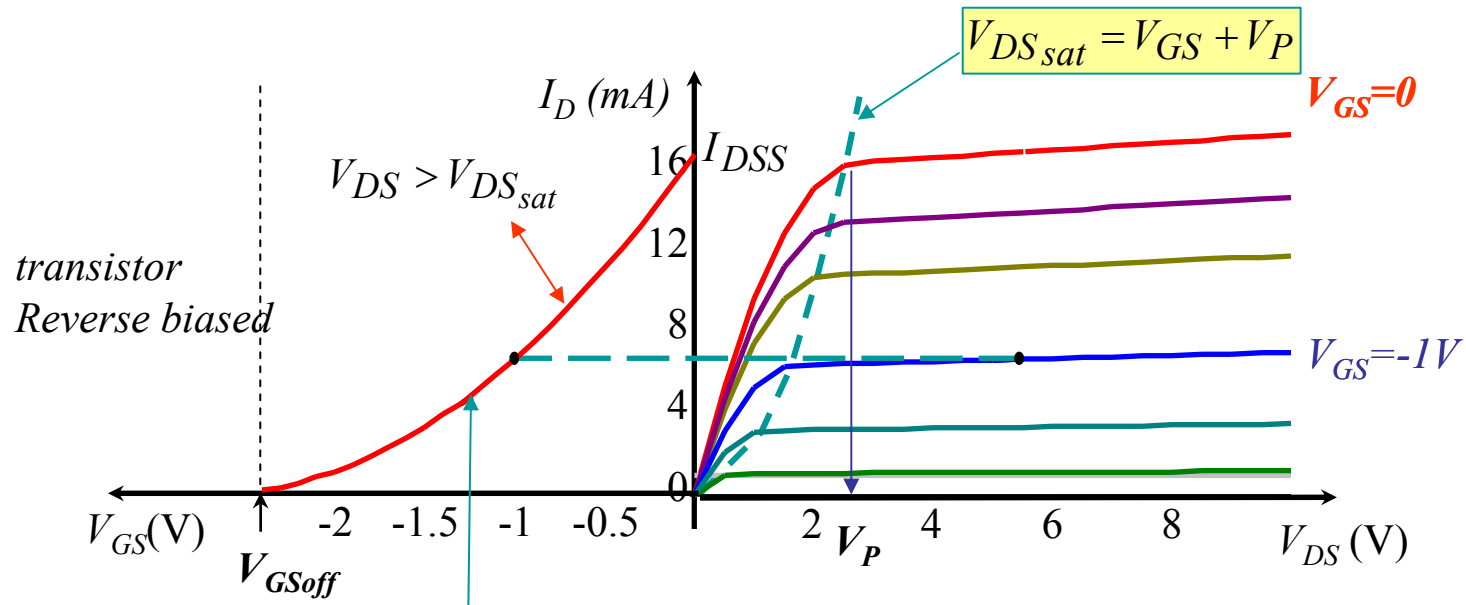

Pinch-off regime for  $V_{DS} > V_{DS_{sat}}$


$$I_D \cong I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS_{off}}} \right)^2 = k (V_{GS} - V_{GS_{off}})^2 \quad k = \frac{I_{DSS}}{V_{GS_{off}}^2}$$

Linear (Ohmic) regime for  $V_{DS} < V_{DS_{sat}}$

$$I_D \cong 2k \left[ (V_{GS} - V_{GS_{off}}) - \frac{V_{DS}}{2} \right] \cdot V_{DS}$$

# FET as control

- When  $V_{GS} \leq V_{GSoff}$ , the channel is depleted → transistor is **blocked**
- When  $V_{GSoff} < V_{GS} < 0$ , and  $V_{DS} > V_{GS} + V_P$ , (with  $V_P \sim |V_{GSoff}|$ ),  
→  $I_D$  saturate and its value is quadratically dependent upon  $V_{GS}$ .
- $V_P$  is the value of  $V_{DS}$  for which  $I_D$  saturates and  $V_{GS}$  is zero.
- The pinch-off regime occurs for  $V_{DS} = V_{GS} + V_P$  ( $V_{GS}$  is non zero)
- For  $0 < V_{DS} \ll V_{GS} + V_P$ ,  $I_D$  is proportional to  $V_{DS}$  (linear regime) and the slope is smaller as  $V_{GS}$  tends toward  $V_{GSoff}$ .

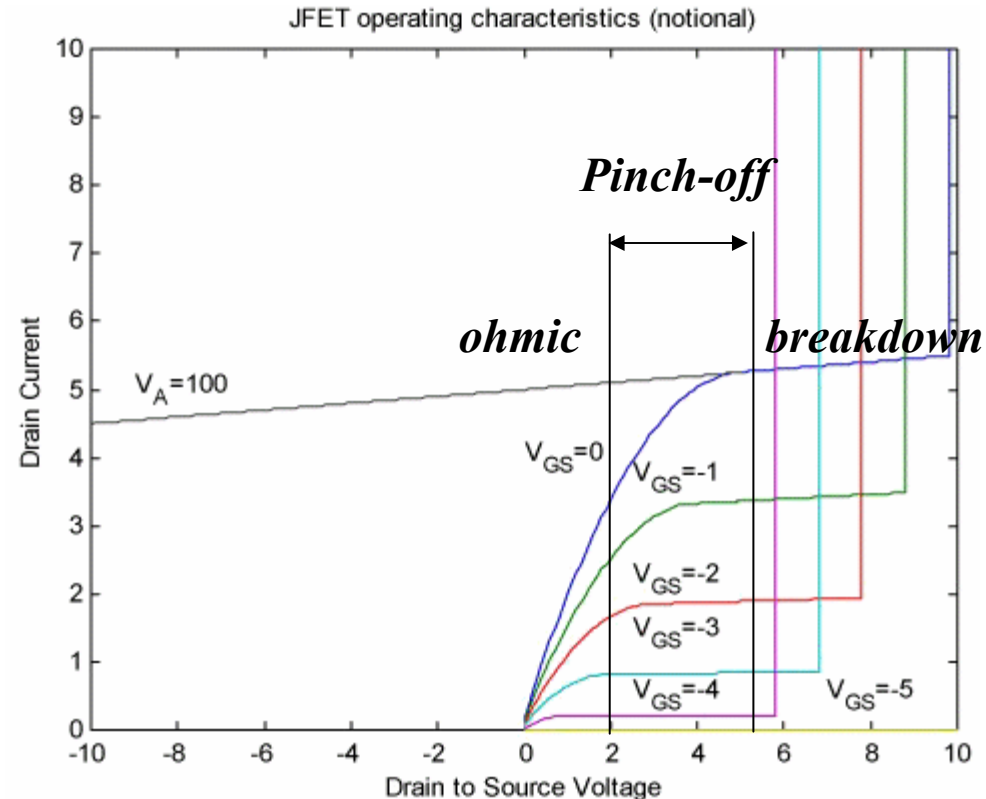


# FET as resistance control

For  $V_{GS} > V_{GSoff}$  and  $V_{DS} < V_{GS} + V_P$ :

$$R_{DS} \cong \frac{1}{k \cdot \left[ (V_{GS} + V_P) - \frac{V_{DS}}{2} \right]}$$

example:

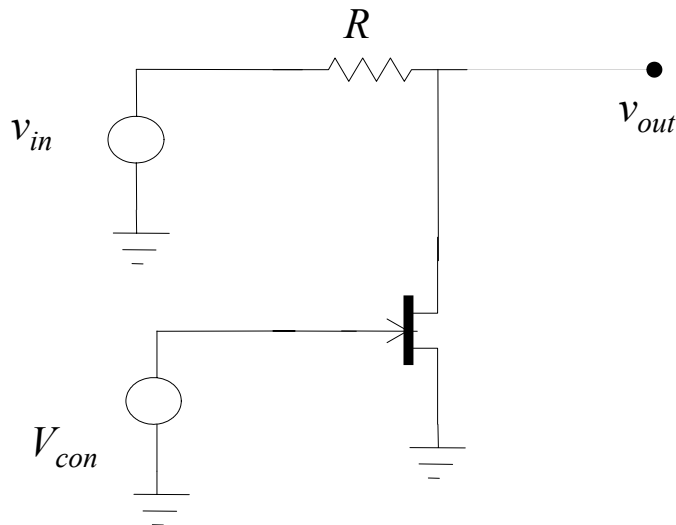

$$\rightarrow v_{out} = \frac{R_{DS}}{R_{DS} + R} v_{in}$$

= variable attenuation **controlled** by  $V_{con}$


Choosing  $R \gg R_{DSon}$ ,  $v_{out}$  varies between  $\sim 0$  et  $v_{in}$

**Problem:**

$R_{DS}$  depends on  $V_{DS} \rightarrow$  nonlinear response
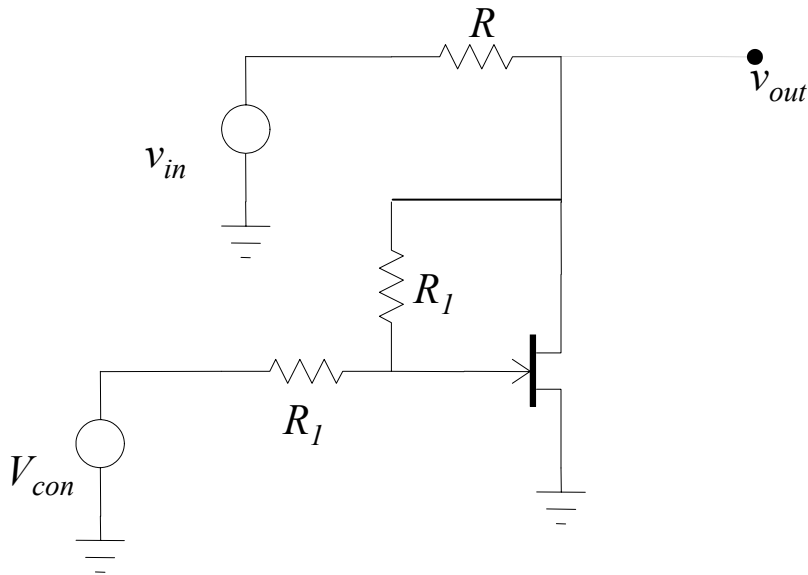
# FET as resistance control: a better solution

$$R_{DS} \cong \frac{1}{k \cdot \left[ (V_{GS} + V_P) - \frac{V_{DS}}{2} \right]}$$



$$\rightarrow V_{GS} = \frac{V_{DS}}{2} + \frac{V_{com}}{2} \quad (I_G \approx 0)$$


$$\rightarrow R_{DS} \approx \frac{1}{k(V_{com} + V_P)}$$

*Better linearity than circuit  
in previous slide*


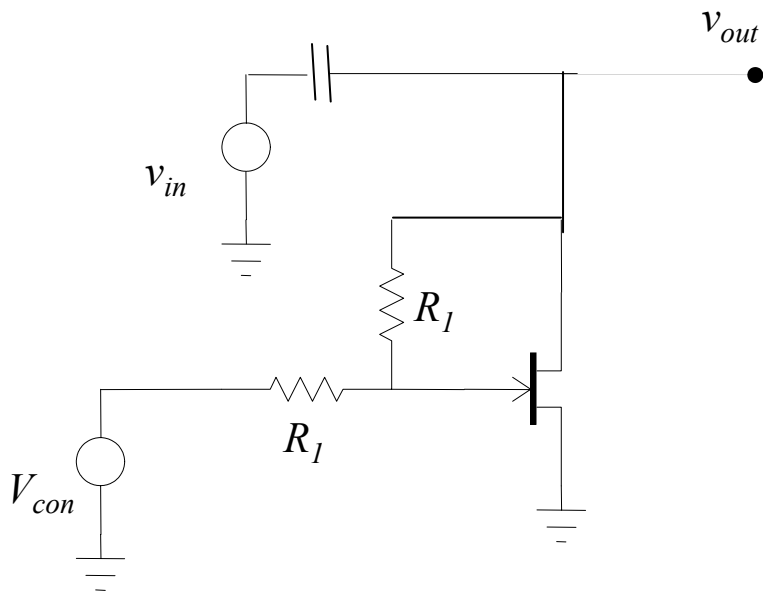
# FET as resistance control: variable frequency filter

- variably controlled resistance in an low (or high) pass filter
- Dynamical adjustment of cut off frequency




$$\rightarrow R_{DS} \approx \frac{1}{k(V_{com} + V_P)}$$

$$\omega \approx \frac{1}{R_{DS}C}$$
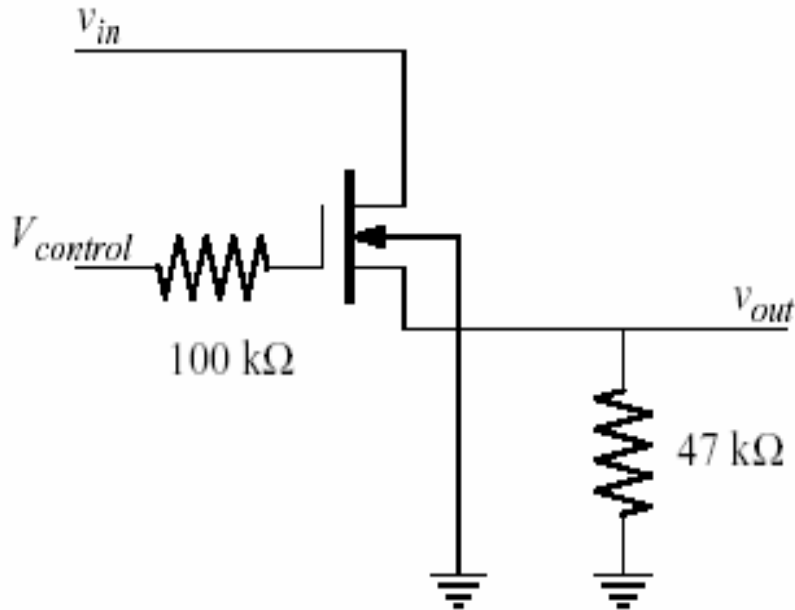
# FET switch based on MOFSET

- Based on a voltage divider 
$$v_{OUT} = \frac{47k\Omega}{R_{DS} + 47k\Omega} v_{in}$$




- When gate at ground

$$R_{DS} > 10^{10} \Omega \Rightarrow v_{OUT} \approx 0$$

- When gate at +15 V

$$R_{DS} \approx 100 \Omega \Rightarrow v_{OUT} \approx v_{in}$$
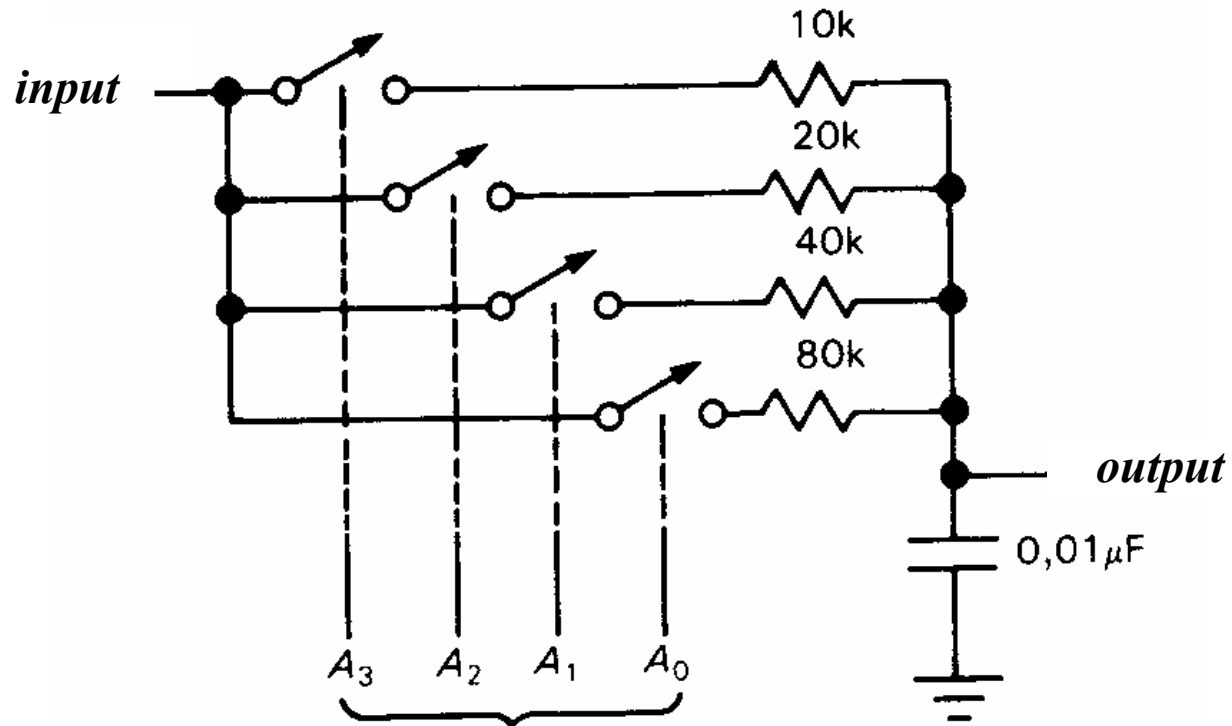
# FET switch based on MOFSET: example of application



*Selection of cut-off frequency*

3-52