


# Alternating & Direct Currents

---

- AC versus DC signals
- AC characterization
- Mathematical tools:
  - Complex number
  - Complex representation of an AC signal
- Resistor in an AC circuit
- Capacitors
- Reactance and Impedance
- RC circuits
- High and low-pass filters

# Alternating Current (AC) versus Direct Current (DC)

---

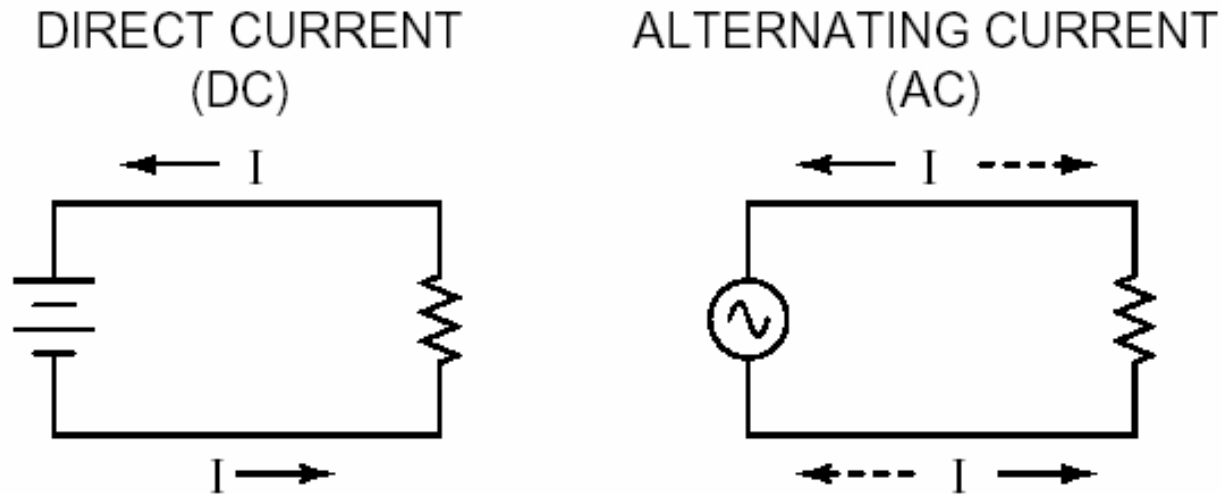

- With AC it is possible to build electric generators, motors and power distribution systems that are far more efficient than DC.
- AC is used predominately across the world of high power


# Alternating Current (AC): waveforms

- AC signals are periodic:

$$S(t + T) = S(t)$$

*period*

Square wave

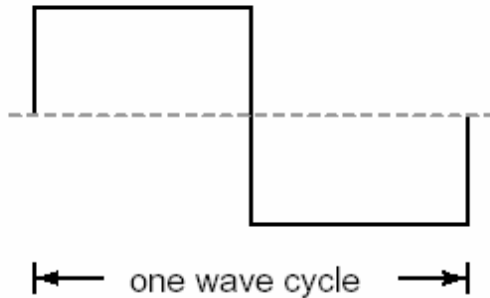


*frequency*

*pulsation*

$$f = \frac{1}{T} = \frac{\omega}{2\pi}$$

Triangle wave

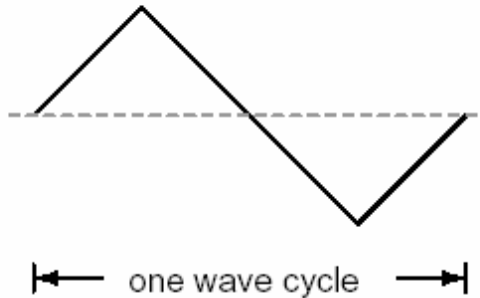


**UNITS:**


*f*: in Hertz (Hz)

*ω*: in  $\text{rad.s}^{-1}$

(the sine wave)

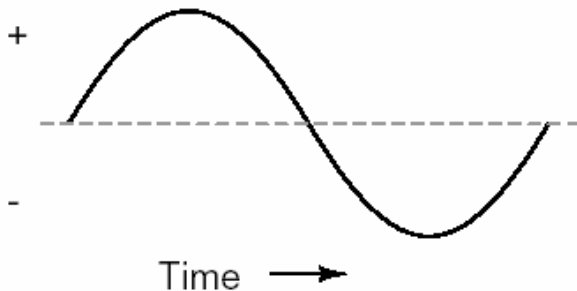


Sawtooth wave

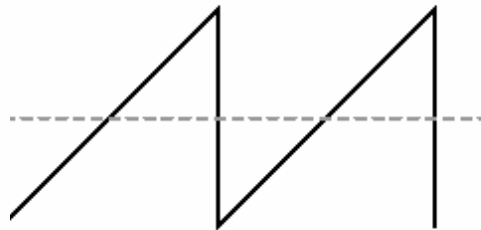


**Heinrich Rudolf Hertz**  
(1857-1894)
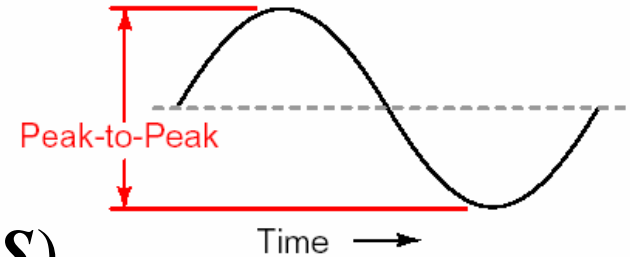
# Alternating Current (AC): characterization

- Can an AC waveform be characterized by few parameters?
- Peak-to-peak (PP)  $PP = \max(S) - \min(S)$



- Peak  $P = \max(S)$

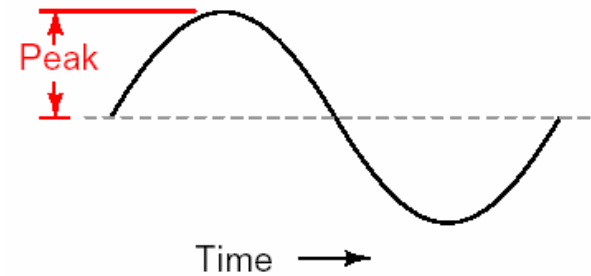

- Average  $\langle S \rangle = \frac{1}{T} \int_t^{t+T} S(t) dt$


- Practical Average

$$AVG = \frac{1}{T} \int_t^{t+T} |S(t)| dt$$

- Root-mean-square

$$RMS \equiv \sqrt{\langle S^2 \rangle - \langle S \rangle^2} = \left[ \frac{1}{T} \int_t^{t+T} S^2(t) dt \right]^{1/2}$$

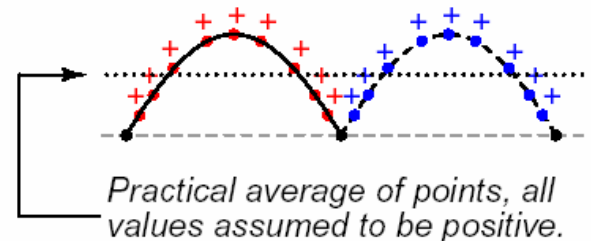True average value of all points (considering their signs) is **zero!**



where

$$\langle S^n \rangle = \frac{1}{T} \int_t^{t+T} S^n(t) dt$$

# Alternating Current (AC): characterization


- For some analytical waveform, there exists relation between the different parameters
- Take a sinusoidal waveform with amplitude 1 then

$$(RMS)^2 = \frac{1}{T} \int_t^{t+T} \sin^2(\omega t) dt = \frac{1}{T} \int_0^{2\pi} \frac{1}{\omega} \sin^2(\vartheta) d\vartheta$$


$$\Rightarrow (RMS) = \frac{\sqrt{2}}{2}$$

$$(AVG) = \frac{1}{T} \int_t^{t+T} |\sin(\omega t)| dt = \frac{1}{T} \int_0^{2\pi} \frac{1}{\omega} |\sin(\vartheta)| d\vartheta$$

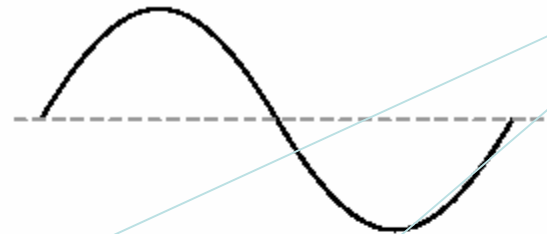
$$= 2 \frac{1}{2\pi} \int_0^{\pi} \sin(\vartheta) d\vartheta = \frac{2}{\pi}$$



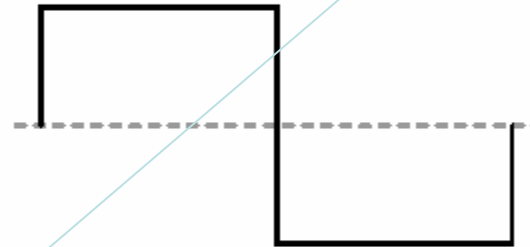
RMS = 0.707 (Peak)  
AVG = 0.637 (Peak)  
P-P = 2 (Peak)



RMS = Peak  
AVG = Peak  
P-P = 2 (Peak)

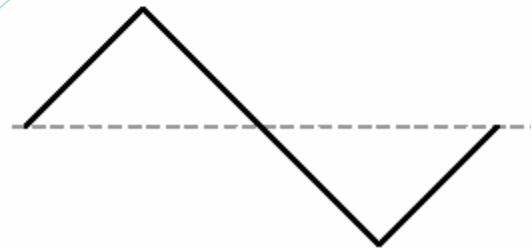

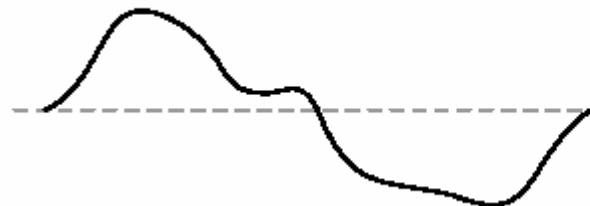
RMS = 0.577 (Peak)  
AVG = 0.5 (Peak)  
P-P = 2 (Peak)



RMS = ???  
AVG = ???  
P-P = 2 (Peak)
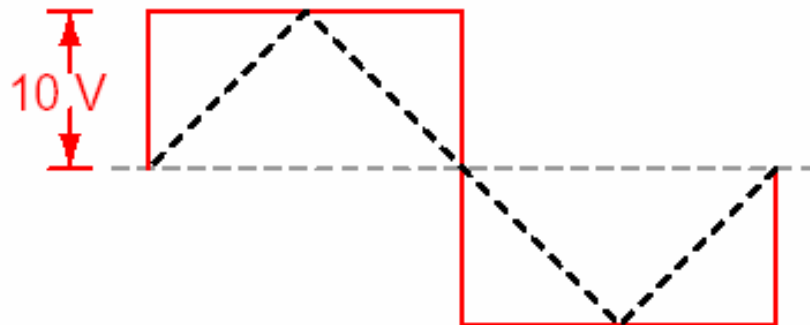
# Alternating Current (AC): characterization

- It matters what waveform is considered
- For instance for the same peak value, a square waveform will result in higher power than a triangular waveform.



Time

(same load resistance)



*more heat energy  
dissipated*



*less heat energy  
dissipated*

# Alternating Current (AC): mathematical tools

---

- In the following we will consider sinusoidal-type waveform (in principle any waveform can be synthesized as a series of sine wave (Fourier)


- We will write (in real notation)

$$S(t) = S_0 \cos(\omega t + \phi)$$


- It often better to use complex notation:

$$S(t) = \Re[S_0 e^{i(\omega t + \phi)}]$$

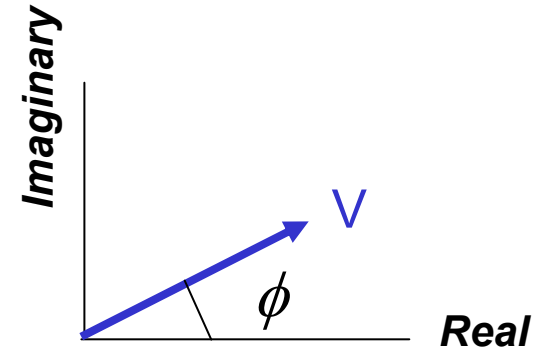- And will often do calculation in complex notation and at the end recall that our physical signal is the real part of the complex results
- We can associate a vector in the complex plane to this complex number





# Resistor in an AC circuit

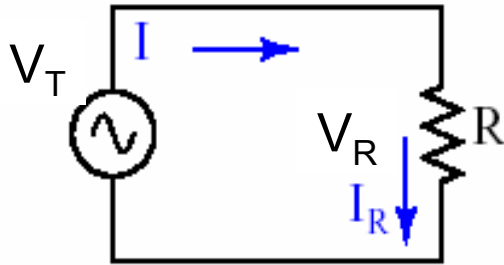

$$V_R = RI_R$$

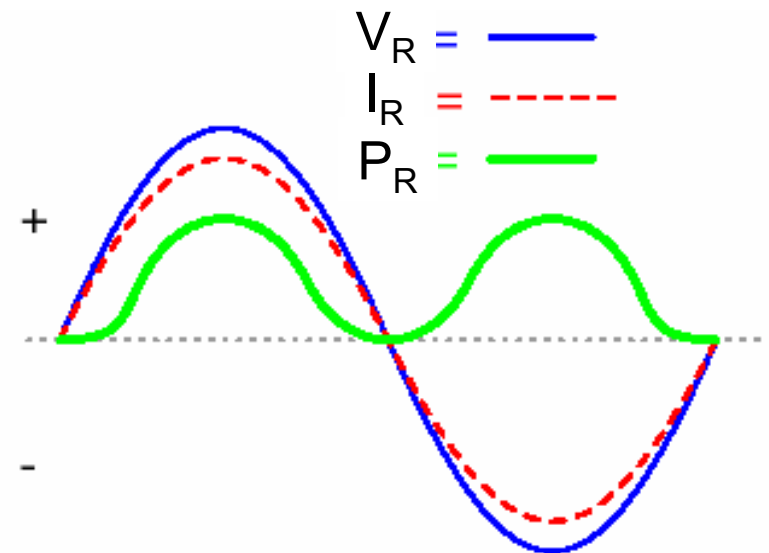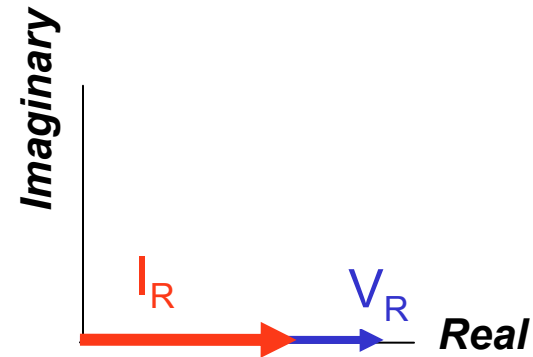- $R$  is a real number. So in the complex plane, all quantities are along real axis
- Current and Voltage are said to be **in phase**
- When instantaneous value of current is zero corresponding instantaneous value of voltage is zero
- Note power  $> 0$  at all time  $\Rightarrow$  resistor always dissipates energy





# Capacitors: voltage versus current relation

- Current induced by electric displacement:.

$$\vec{J} = \frac{\partial \vec{D}}{\partial t} = \epsilon \frac{\partial \vec{E}}{\partial t} + \frac{\partial \vec{P}}{\partial t}$$



- Assume a simple model of two plate separated by a small distance. Gauss's law gives:

$$\oint \vec{E} \cdot d\vec{S} = \frac{Q}{\epsilon_0} \Rightarrow E = \frac{Q}{\epsilon_0 A}$$

$$\Rightarrow V = \frac{QL}{\epsilon_0 A} \equiv \frac{Q}{C}$$

*capacitance*
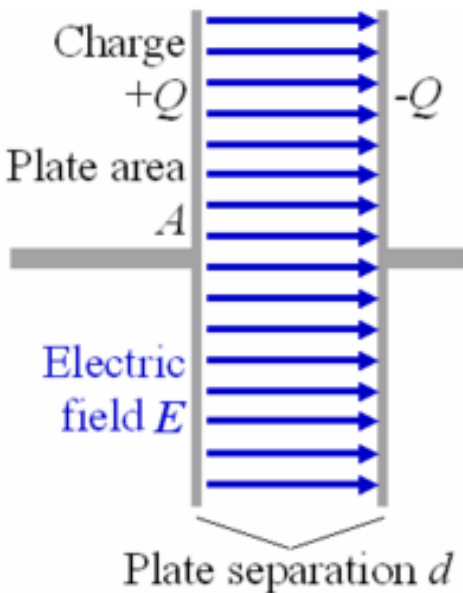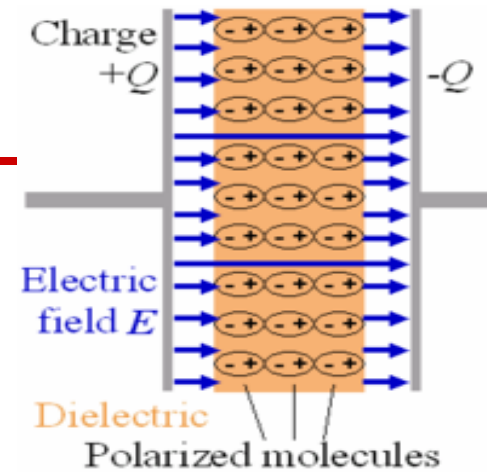
$$\vec{J} = \epsilon_0 \frac{\partial \vec{E}}{\partial t} \Rightarrow \frac{\partial V}{\partial t} = \frac{Jd}{\epsilon_0} = \frac{Id}{A\epsilon_0} = \frac{1}{C} I \Leftrightarrow I = C \frac{\partial V}{\partial t}$$





# Capacitors: technical aspects


- Unit for Capacitance is Farad (in honor to Faraday)

- Capacitor symbol:


- Capacitor symbols*

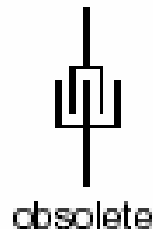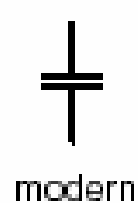

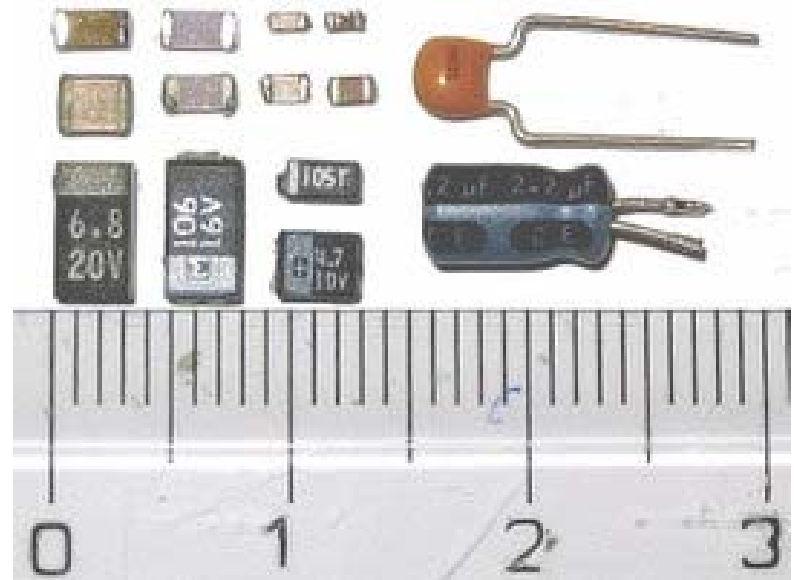- Real world capacitors also introduce a resistance (we will ignore this effect)



*Capacitor equivalent circuit*

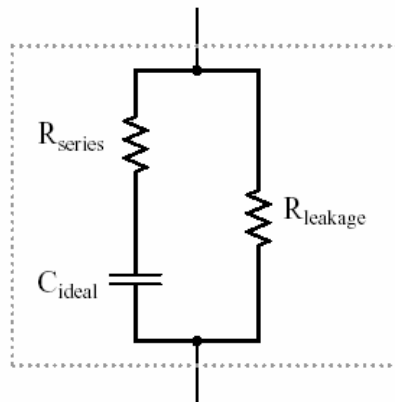


*M. Faraday (1791-1867)*
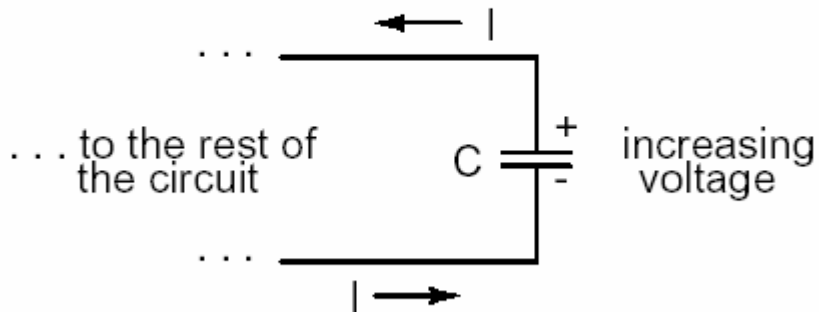
# Capacitor


- A capacitor either acts as a load or as a source

*Energy being absorbed by the capacitor from the rest of the circuit.*



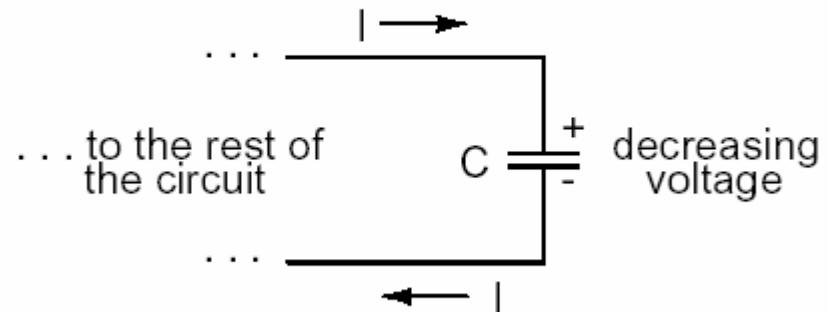**The capacitor acts as a LOAD**


*Energy being released by the capacitor to the rest of the circuit*



**The capacitor acts as a SOURCE**


- A capacitor can therefore store energy.

# Capacitor in an AC circuits

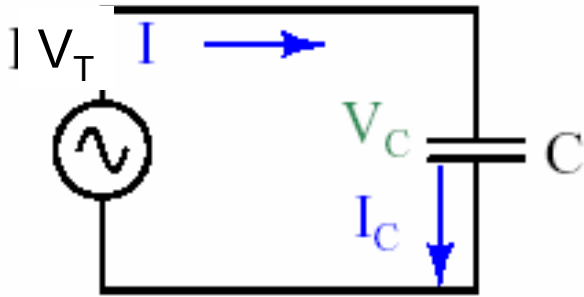

$$I_C = C \frac{dV_C}{dt} = i\omega C V_C$$

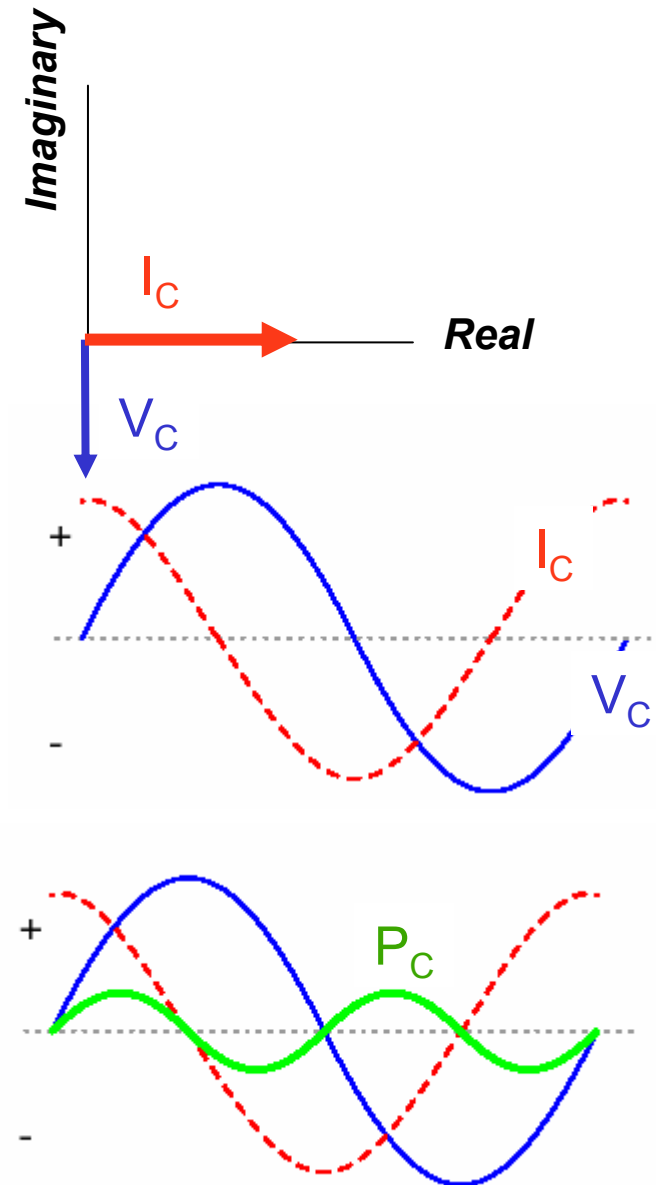- Capacitors do not behave the same as resistors
- Resistors allow a flow of e- proportional to the voltage drop
- Capacitors oppose change by drawing or supplying current as they charge or discharge.



# Reactance and Impedance

---


- The general linear relation between  $V$  and  $I$  is of the form

$$\mathbf{Z} \equiv \mathbf{V} / \mathbf{I}$$

$Z$  is called **impedance**.

- For a resistor  $Z=R$  is a **real number**.
- For a capacitor  $Z = \frac{-i}{\omega C}$  is an **imaginary number**
- Generally  $Z$  will be a **complex number** (if  $V$  and  $I$  are written in their complex forms)
- For instance if a circuit has both capacitor(s) and resistor(s) we expect  $Z$  to generally be a complex number
- For a capacitor the quantity  $X_c = \frac{-1}{\omega C}$  is called reactance and is in Ohm ( $\Omega$ )
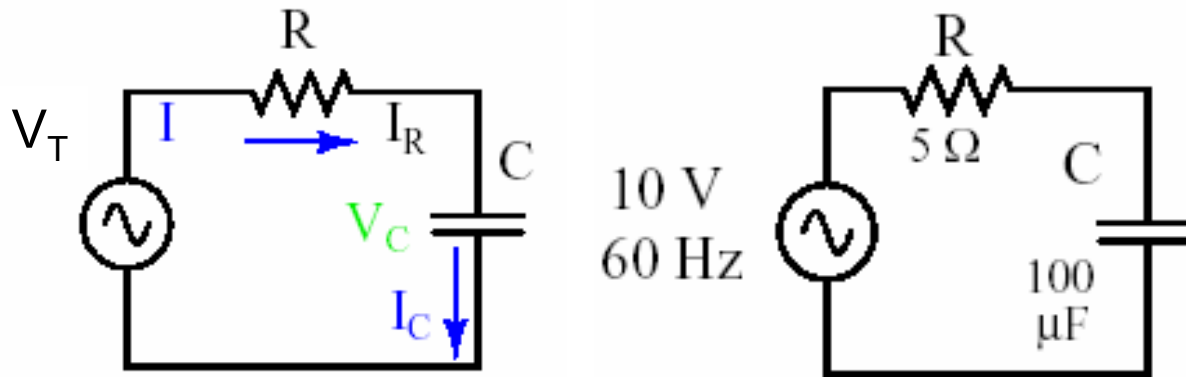
# Example: Impedance of a series RC Circuits



- Let's compute the total impedance of the RC circuit:


$$V_T = V_C + V_R = \frac{-i}{\omega C} I + RI = \left(R - \frac{i}{\omega C}\right) I$$

$$\Rightarrow Z = R - \frac{i}{\omega C} = R + iX_C$$



- The impedance can be written as:

$$Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} e^{i\Xi}, \text{ with } \tan \Xi = -\frac{1}{\omega RC}$$

- NA:  $Z = 5 - 26.52i$  or  $|Z| = 29.99$  and  $\Xi = -79.325$  degree

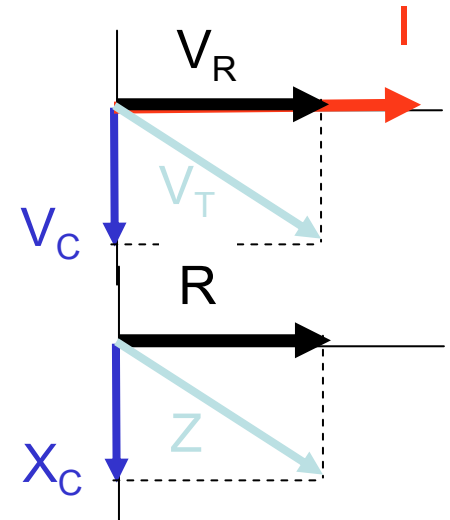
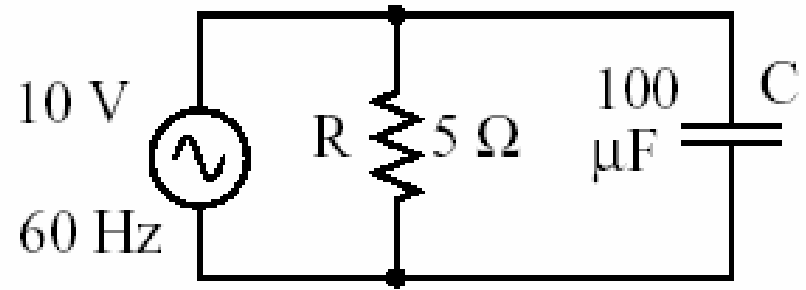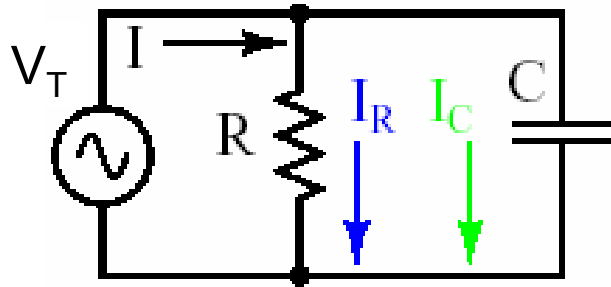
# Example: Impedance of a parallel RC Circuits




- Let's compute the total impedance of the RC circuit:

$$I = I_C + I_R = \left( i\omega C + \frac{1}{R} \right) V$$


$$\Rightarrow Z = \left( i\omega C + \frac{1}{R} \right)^{-1} = \frac{1}{\frac{1}{X_C} + \frac{1}{R}}$$

- NA:  $Z = 4.83 - 0.91i$  or  $|Z| = 4.91$  and  $\angle = -10.68$  degree

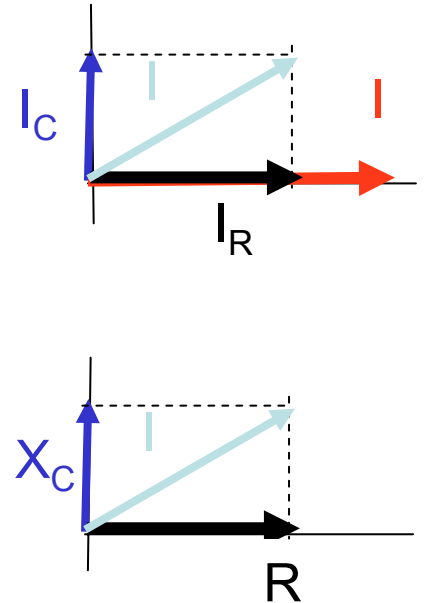

# General Analysis of an RC series circuits

---

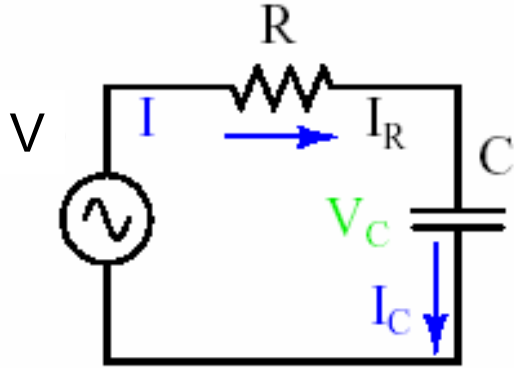

$$V = V_0 \cos \omega t = \Re(V_0 e^{i\omega t})$$

- Let's write the ODE for the current

$$V = V_R + V_C = RI + \int \frac{I}{C} dt$$

$$\Leftrightarrow \frac{dI}{dt} + \frac{1}{RC} I = \frac{1}{R} \frac{dV}{dt}$$

- How do we solve?



# Solving the differential equation for the RC series circuit

---

- Previous equation is of the form:

$$y'(t) + \alpha y(t) = f(t), \quad y(0) = y_0$$

- First find the solution for the homogeneous equation

$$y_h = D e^{-\alpha t}$$

- Then find a particular solution of the inhomogeneous equation  $y_p(t) = g(t) e^{-\alpha t}$

$$f(t) = (g(t) e^{-\alpha t})' + \alpha g(t) e^{-\alpha t}, \Rightarrow f(t) = g'(t) e^{-\alpha t}$$

$$g(t) = \int_0^t f(s) e^{\alpha s} ds$$

- The general solution is of the form  $y_g = y_h + y_p = e^{-\alpha t} (D + \int_0^t f(s) e^{\alpha s} ds)$

- So finally we have

$$y(t) = e^{-\alpha t} (y_0 + \int_0^t f(s) e^{\alpha s} ds)$$

# General Analysis of an RC series circuits

---


- Applying previous results to RC series circuits gives:

$$I(t) = \frac{V_0}{R} e^{-\frac{t}{RC}} \left( 1 + \frac{\omega^2 + \frac{i\omega}{RC}}{\omega^2 + \frac{1}{R^2 C^2}} \left( e^{i\omega t + \frac{t}{RC}} - 1 \right) \right)$$


- Or in real notations:

$$I(t) = \frac{V_0}{R} \left( 1 - \frac{\omega^2}{\omega^2 + \frac{1}{R^2 C^2}} \right) e^{-\frac{t}{RC}} + \frac{V_0}{R} \frac{\omega^2}{\omega^2 + \frac{1}{R^2 C^2}} \cos \omega t - \frac{V_0}{R^2 C} \frac{\omega}{\omega^2 + \frac{1}{R^2 C^2}} \sin \omega t$$
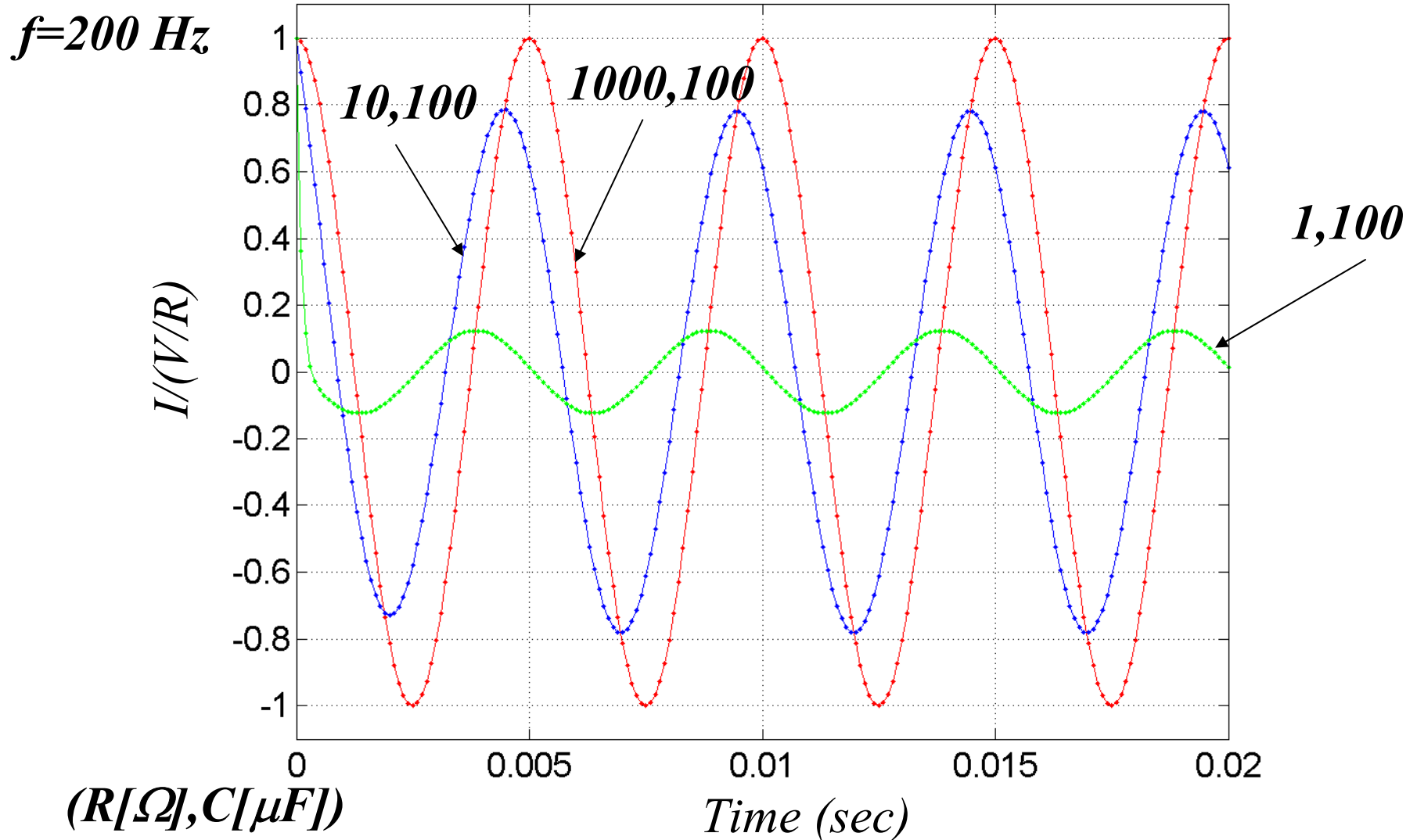
# General Analysis of an RC series circuits


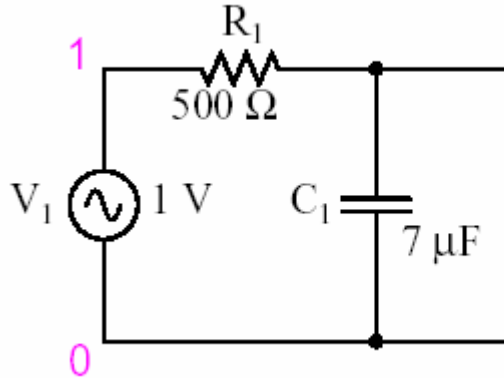
# RC series circuits as frequency filters: low pass



- The voltage across capacitor is

$$V_c = -\frac{i}{\omega C} I = -\frac{i}{\omega C} \frac{V}{Z}$$
$$\Rightarrow V_c = \frac{1 - iRC\omega}{1 + R^2 C^2 \omega^2} V$$


- The gain  $A$  is defined as:  $A = |A| e^{i\Theta}$

$$A = \frac{V_c}{V} = \frac{1 - iRC\omega}{1 + R^2 C^2 \omega^2}$$
$$\Rightarrow |A| = \frac{1}{\sqrt{1 + R^2 C^2 \omega^2}}; \Theta = \arctan(-RC\omega)$$


- Note the limits

$$\lim_{\omega \gg 1/RC} |A| = 0; \quad \lim_{\omega \ll 1/RC} |A| = 1$$
$$\lim_{\omega \gg 1/RC} \Theta = -90; \quad \lim_{\omega \ll 1/RC} \Theta = 0$$

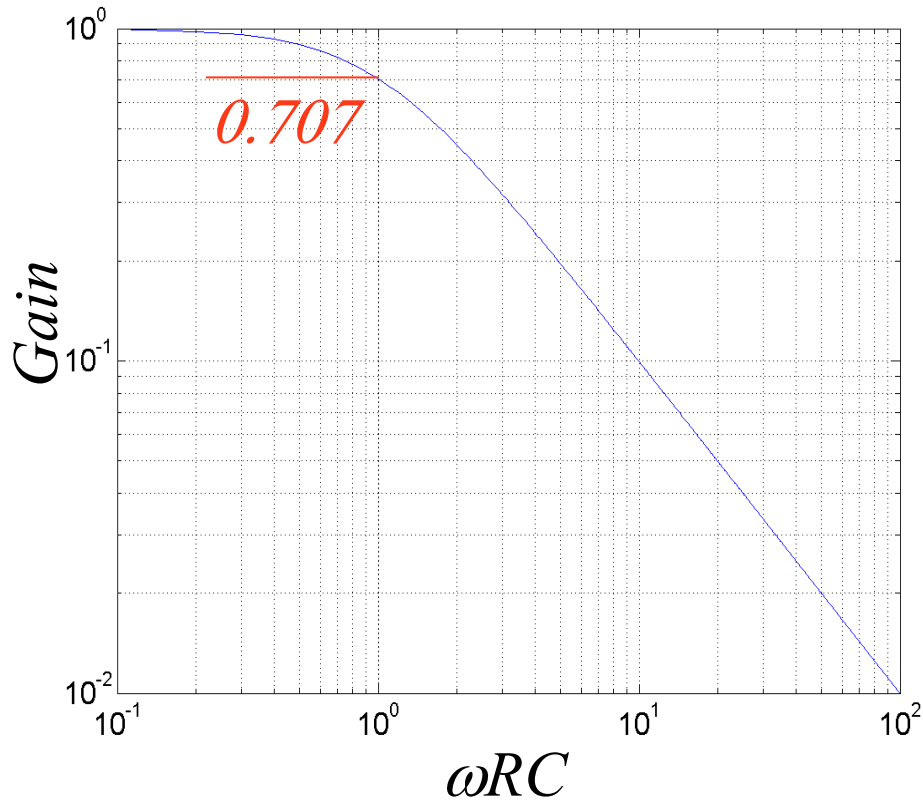
# RC series circuits as frequency filters: low pass



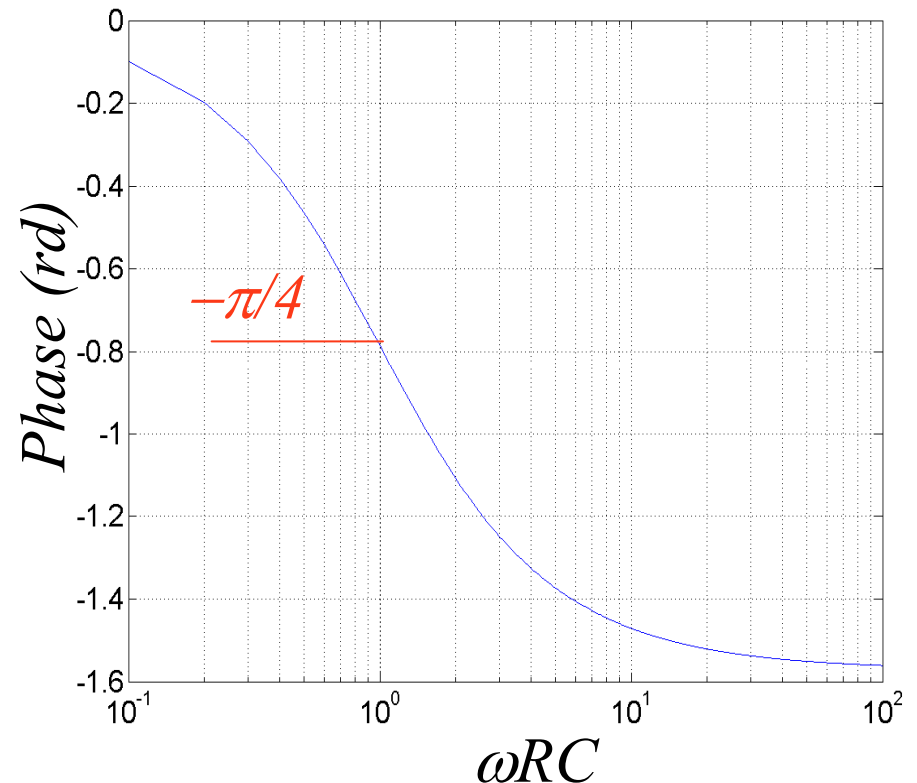- Signal with frequencies **below**  $1/RC$  are **unaltered**,
- Signal with frequency **above**  $1/RC$  are **attenuated**


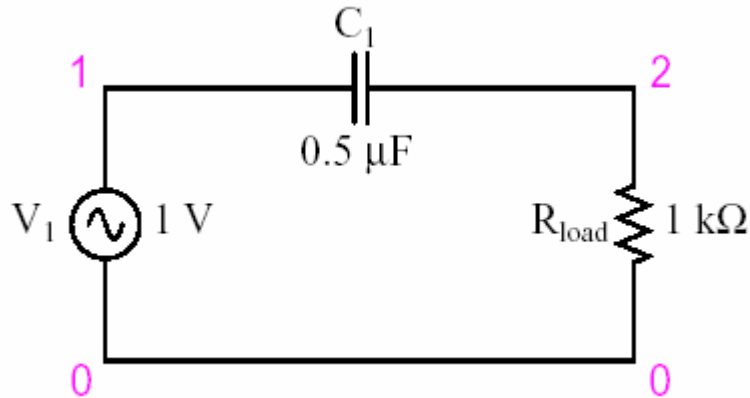
# RC series circuits as frequency filters: high pass



- The voltage across capacitor is

$$V_R = RI = R \frac{V}{Z}$$
$$\Rightarrow V_c = R \frac{1}{R - \frac{i}{C\omega}} V$$



- The gain  $A$  is defined as:  $A = |A| e^{i\Theta}$

$$A = \frac{V_c}{V} = \frac{R^2 C^2 \omega^2 + iRC\omega}{1 + R^2 C^2 \omega^2}$$
$$\Rightarrow |A| = \frac{RC\omega}{\sqrt{1 + R^2 C^2 \omega^2}}; \Theta = \arctan\left(\frac{1}{RC\omega}\right)$$

- Note the limits

$$\lim_{\omega \gg 1/RC} |A| = 1; \quad \lim_{\omega \ll 1/RC} |A| = RC\omega$$
$$\lim_{\omega \gg 1/RC} \Theta = 0; \quad \lim_{\omega \ll 1/RC} \Theta = 90$$
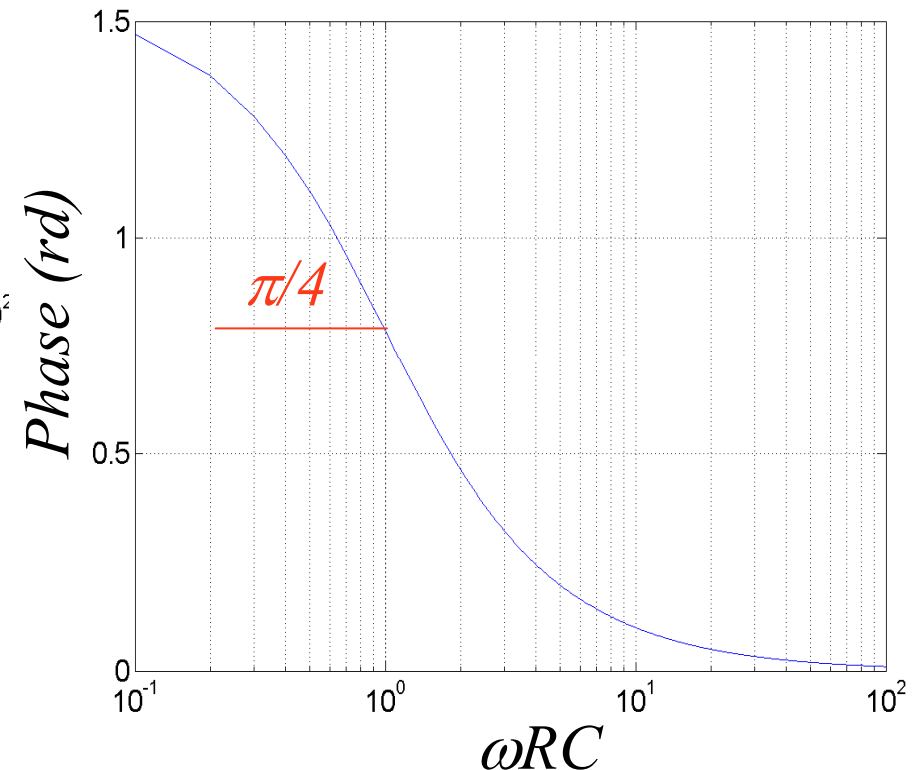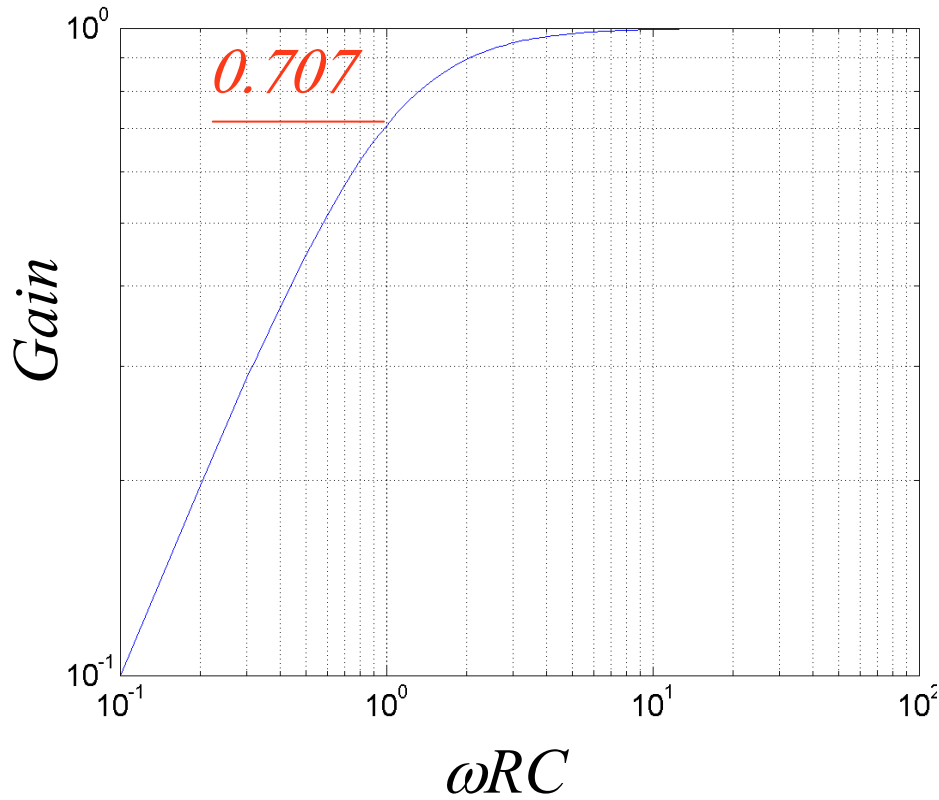
# RC series circuits as frequency filters: high pass



- Signal with frequencies **above**  $1/RC$  are **unaltered**,
- Signal with frequency **below**  $1/RC$  are **attenuated**