
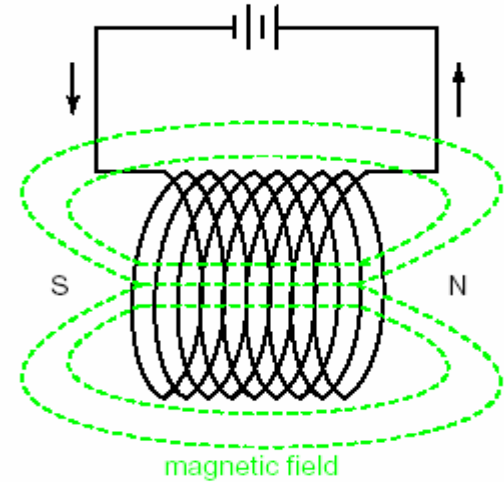


Lesson 3: RLC circuits & resonance

- Inductor, Inductance
- Comparison of Inductance and Capacitance
- Inductance in an AC signals
- RL circuits
- LC circuits: the electric “pendulum”
- RLC series & parallel circuits
- Resonance

Inductor

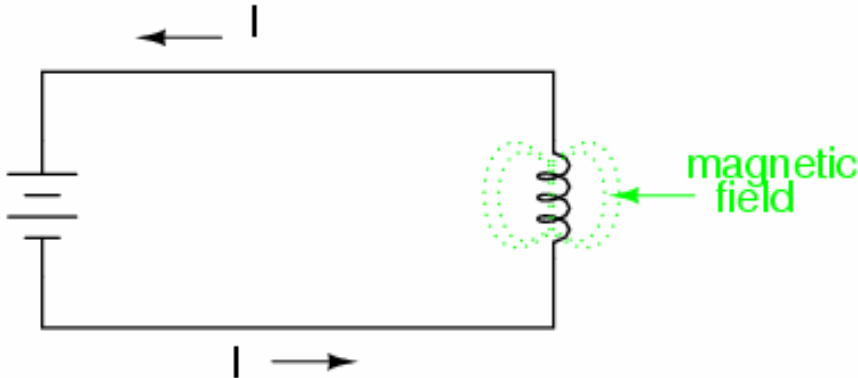

- Start with Maxwell's equation $\vec{\nabla} \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$
- Integrate over a surface S (bounded by contour C) and use Stoke's theorem:

$$\iint_S \vec{\nabla} \times \vec{E} \cdot d\vec{A} = \oint_{S \in C} \vec{E} \cdot d\vec{l} = - \iint_S \frac{\partial \vec{B}}{\partial t} \cdot d\vec{A} = - \frac{\partial \Phi}{\partial t}$$

- The voltage is thus

$$V_L = -emf = \frac{\partial \Phi}{\partial t}$$

Magnetic flux in Weber



Wilhelm Weber (1804-1891)

Inductor

- Now need to find a relation between magnetic field generated by a loop and current flowing through the loop's wire. Used Biot and Savart's law:

$$d\vec{B} = \frac{\mu_0}{4\pi} I d\vec{l} \times \frac{\hat{r}}{r^2} \Rightarrow \mathbf{B} \propto \mathbf{I}$$

- Integrate over a surface S the magnetic flux is going to be of the form

$$\Phi \equiv LI$$

*Inductance measured
in Henri (symbol H)*

- The voltage is thus

$$V_L = \frac{\partial \Phi}{\partial t} = L \frac{dI}{dt}$$



Joseph Henri (1797-1878)

Inductor

- Case of loop made with an infinitely thin wire

$$B = \frac{\mu}{4\pi} \oint dl \cdot I$$

- If the inductor is composed of n loop per meter then total B-field is

$$B = \frac{\mu}{4\pi} nI$$

- So inductance is

$$\Phi \equiv BA = \frac{\mu}{4\pi} AnI \Rightarrow L = \frac{\mu}{4\pi} An$$

Area of the loop



Increase magnetic permeability (e.g. use metallic core instead of air)

Increase number of wire per unit length increase L

Inductor in an AC Circuit


$$V_L = L \frac{dI}{dT}$$
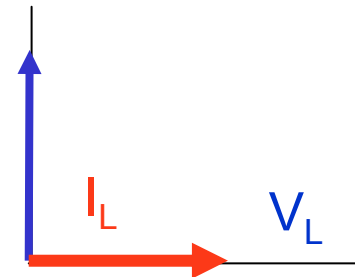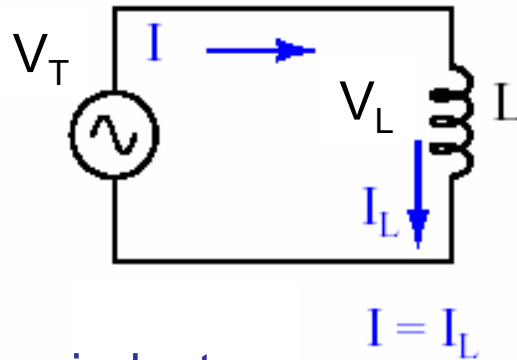
$$\Rightarrow Z = \frac{V_L}{I} = i\omega L$$



- Introduce reactance for an inductor:

$$X_L = \omega L$$

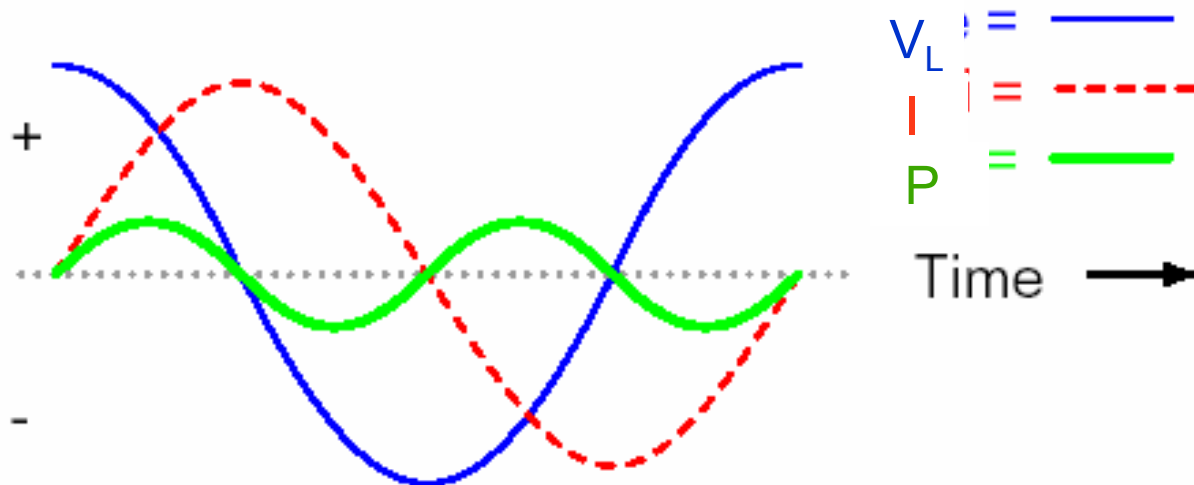

Inductor , Capacitor, Resistor


- Resistance = friction against motion of electrons
- Reactance = inertia that opposes motion of electrons

$$X_L = \omega L$$

$$X_C = -\frac{1}{\omega C}$$

- Impedance is a generally complex number:


$$Z = R + iX$$

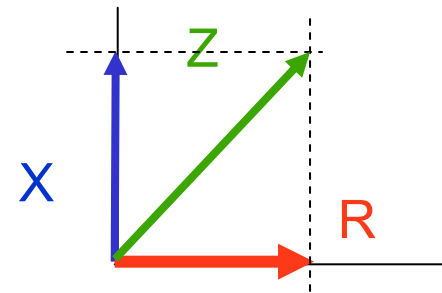



- Note also one introduces the Admittance:

$$Y = \frac{1}{Z} = G + iB$$

\nearrow
conductance
 \nwarrow
susceptance


Resistor	100 Ω
	$R = 100 \Omega$ $X = 0 \Omega$ $Z = 100 \Omega \angle 0^\circ$

Inductor	100 mH 159.15 Hz
	$R = 0 \Omega$ $X = 100 \Omega$ $Z = 100 \Omega \angle 90^\circ$

Capacitor	10 μF 159.15 Hz
	$R = 0 \Omega$ $X = 100 \Omega$ $Z = 100 \Omega \angle -90^\circ$


Inductor versus Capacitor

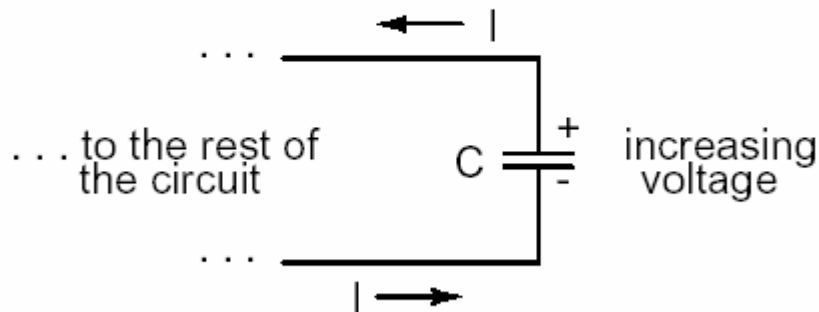Energy being absorbed by the capacitor from the rest of the circuit.




The capacitor acts as a LOAD

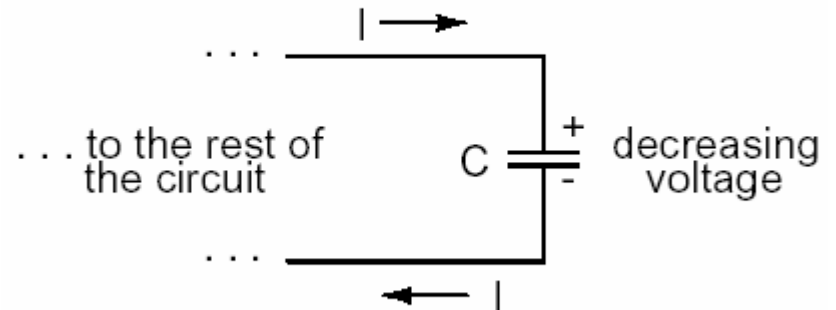Energy being released by the capacitor to the rest of the circuit




The capacitor acts as a SOURCE

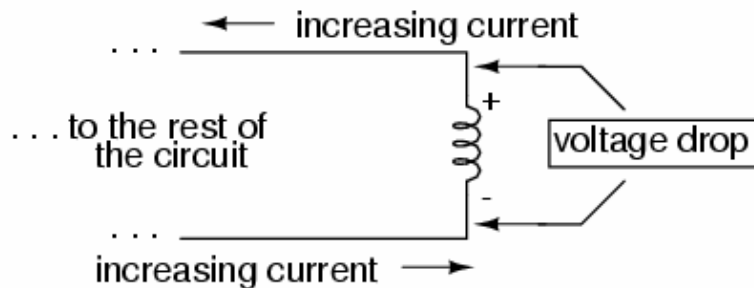Energy being absorbed by the inductor from the rest of the circuit.



The inductor acts as a LOAD

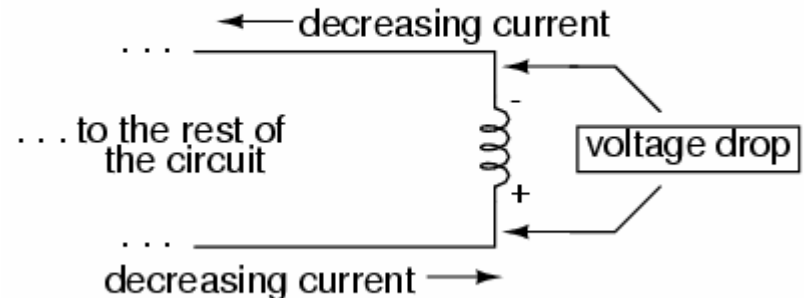
Energy being released by the inductor to the rest of the circuit.



The inductor acts as a SOURCE

RL series Circuits
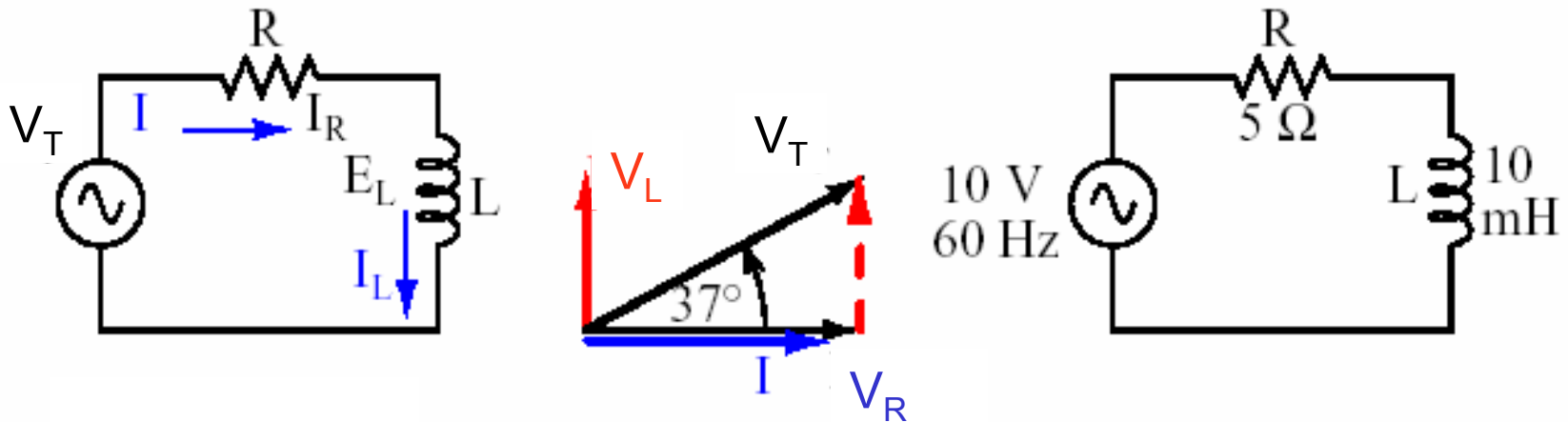
$$V_T = V_R + V_L = RI + L \frac{dI}{dt} = (R + i\omega L)I \Rightarrow Z = R + i\omega L = R + iX_L$$




- For the above circuit we can compute a numerical value for the impedance:

$$Z = (5 + 3.7699i) \quad \Omega$$

$$|Z| = \sqrt{5^2 + 3.7699^2} \approx 6.262, \quad \Theta = 37.02^\circ$$

RL parallel Circuits
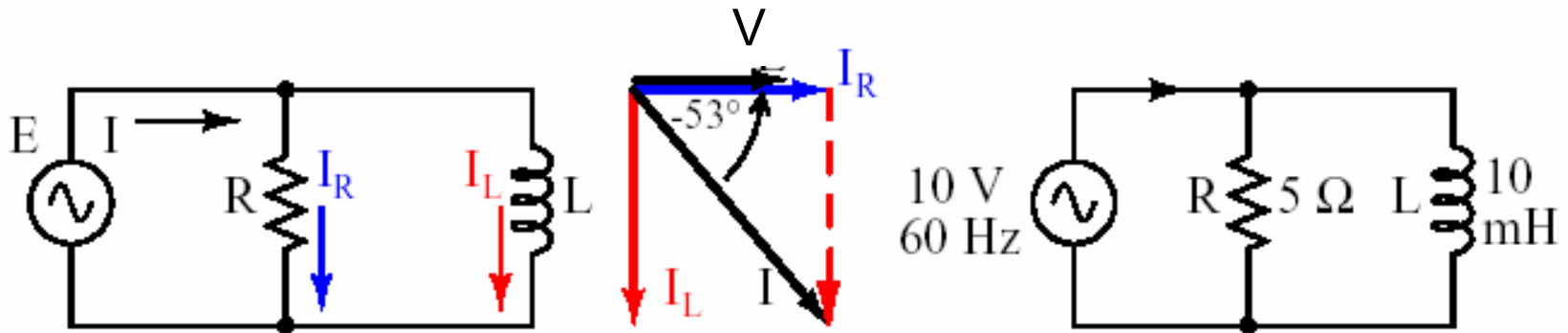
$$I = I_R + I_L = \frac{V}{R} + \frac{1}{L} \int V dt = \left(\frac{1}{R} + \frac{1}{i\omega L} \right) V \Rightarrow Z^{-1} = R^{-1} + (i\omega L)^{-1}$$



- For the above circuit we can compute a numerical value for the impedance:

$$Z = (1.81 + 2.40i) \quad \Omega$$


$$|Z| \approx 3.01, \quad \Theta = 52.98^\circ$$

Inductor: Technical aspects


- Inductors are made a conductor wired around air or a ferromagnetic core
- Unit of inductance is Henri, symbol is H
- Real inductors also have a resistance (in series with inductance)





Inductor symbols

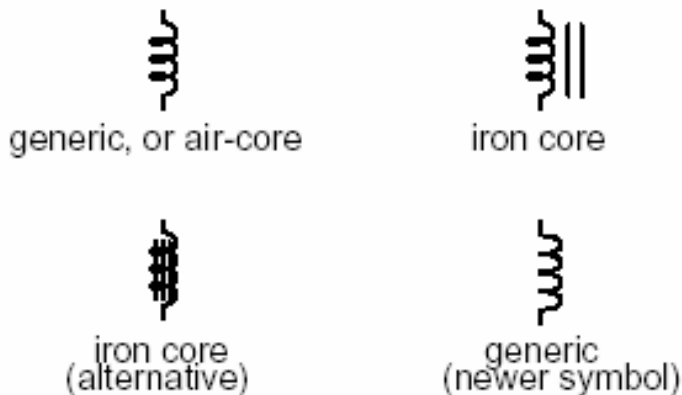

Equivalent circuit for a real inductor

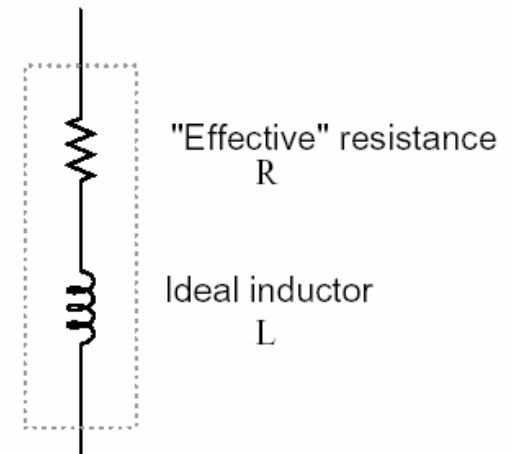


RLC series/parallel Circuits

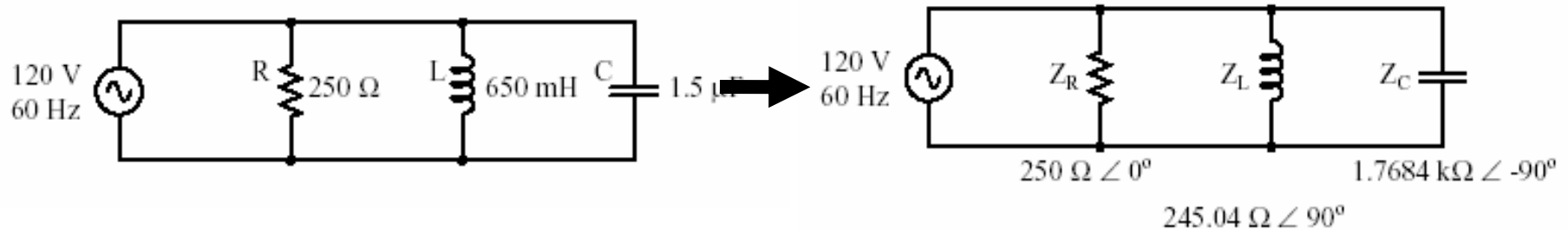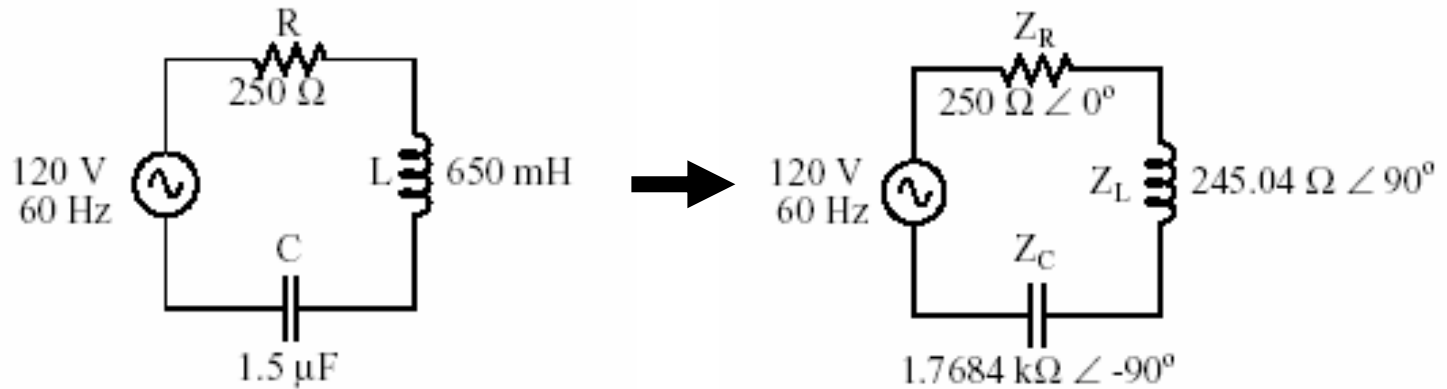

RLC series/parallel Circuits: an example

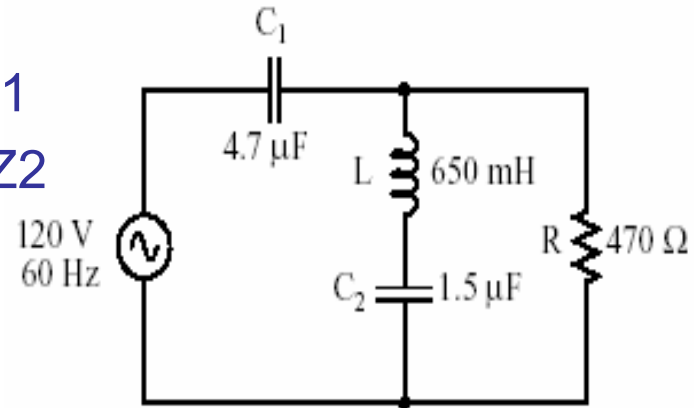- Compute impedance of the circuit below
 - Step 1: consider C2 in series with L $\Rightarrow Z_1$
 - Step 2: consider Z1 in parallel with R $\Rightarrow Z_2$
 - Step 3: consider Z2 in series with C
- Let's do this:











$$Z_1 = i \left(L\omega - \frac{1}{C\omega} \right) = 1523.34i \quad Z_2 = \frac{1}{\frac{1}{Z_1} + \frac{1}{R}} = 429.15 - 132.41i$$
$$Z_3 = Z_2 - \frac{i}{C_1\omega} = 429.15 - 629.79i$$

- Current in the circuit is

$$I = \frac{V}{Z_3} = 76.89 + 124.86i \Rightarrow |I| = 146.64 \text{ mA}, \angle I = 58.371^\circ$$


- And then one can get the voltage across any components

LC circuit: An electrical pendulum

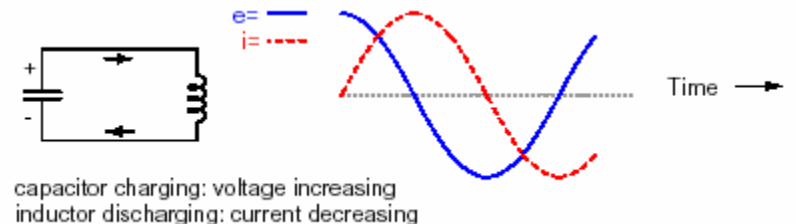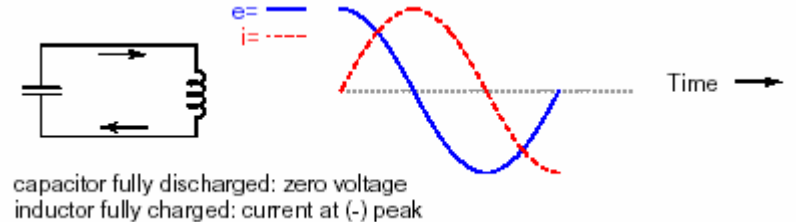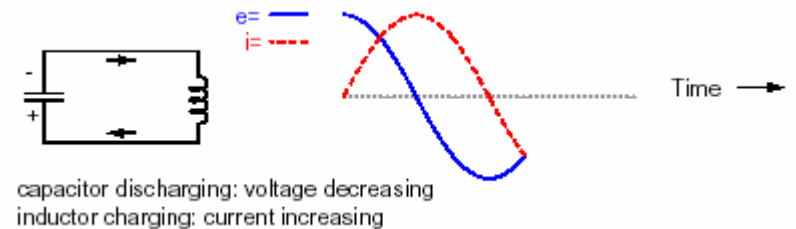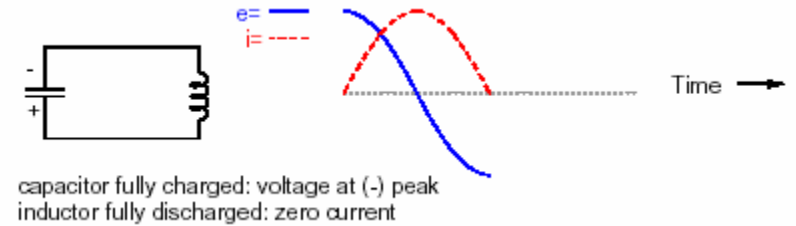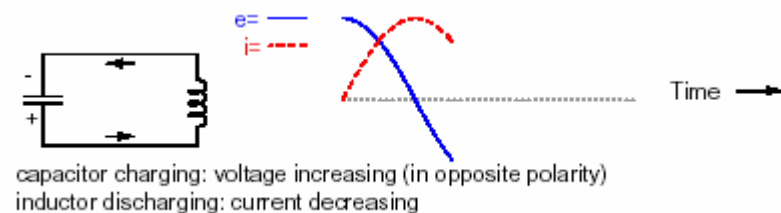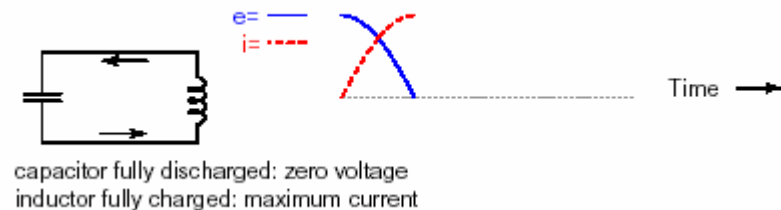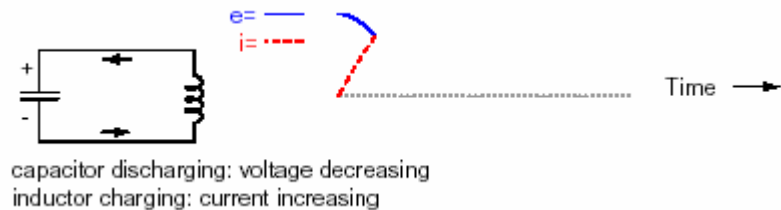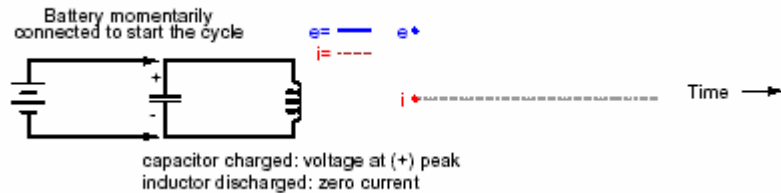

LC circuit: An electrical pendulum

- Mechanical pendulum: oscillation between potential and kinetic energy
- Electrical pendulum: oscillation between magnetic ($\frac{1}{2}LI^2$) and electrostatic ($\frac{1}{2}CV^2$) energy
- In practice, the LC circuit showed has some resistance, i.e. some energy is dissipated and therefore the oscillation amplitude is damped. The oscillation frequency keeps unchanged.
- LC circuit are sometime called tank circuit and oscillate (=resonate)

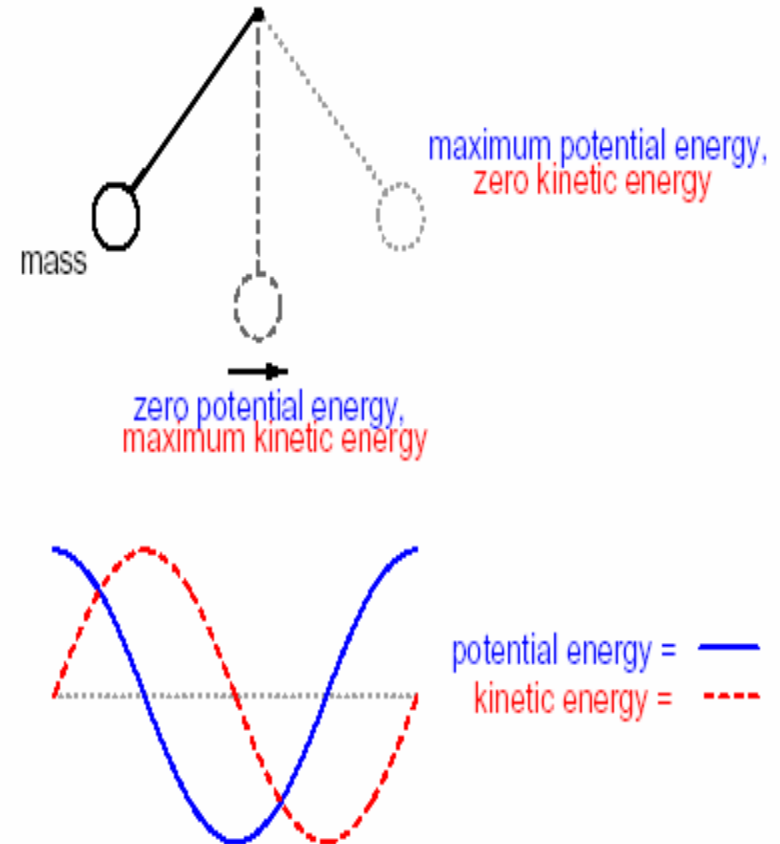


Example of a simple “tank” (LC) circuit

- ODE governing this circuit?

$$I = I_C + I_L = C \frac{dV}{dt} + \frac{1}{L} \int V dt$$
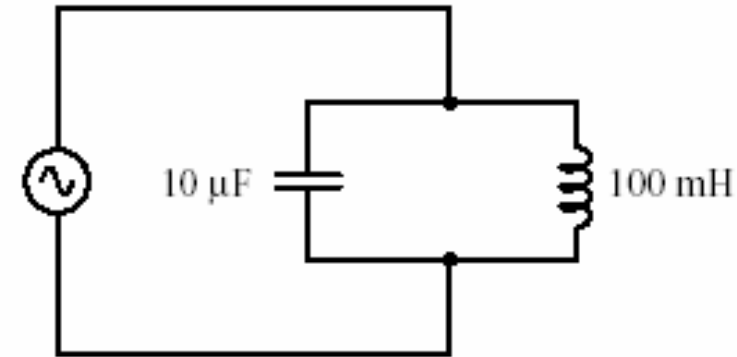
$$\frac{dI}{dt} = C \frac{d^2 V}{dt^2} + \frac{1}{L} V \Leftrightarrow \boxed{\frac{d^2 V}{dt^2} + \frac{1}{LC} V = \frac{dI}{dt}}$$



- Equation of a simple harmonic oscillator with pulsation:

$$\omega = \frac{1}{\sqrt{LC}}$$


- Or one can state that system oscillate if impedance associated to C and L are equal, i.e.:

$$L\omega = \frac{1}{C\omega}$$

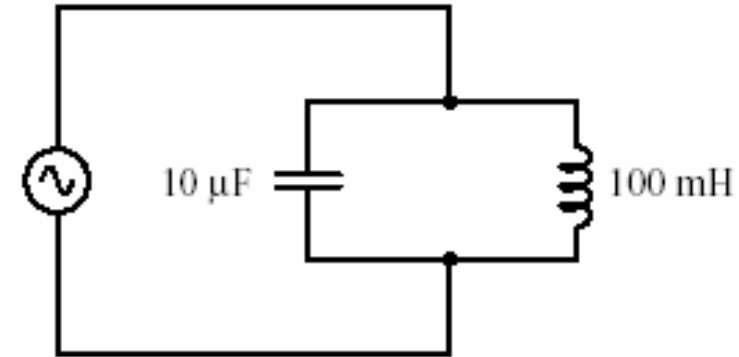
Example of a simple “tank” (LC) circuit

- What is the total impedance of the circuits?

$$Z^{-1} = iL\omega - \frac{i}{C\omega} = i(L\omega - \frac{1}{L\omega}) = 0 \Rightarrow Z = \infty$$



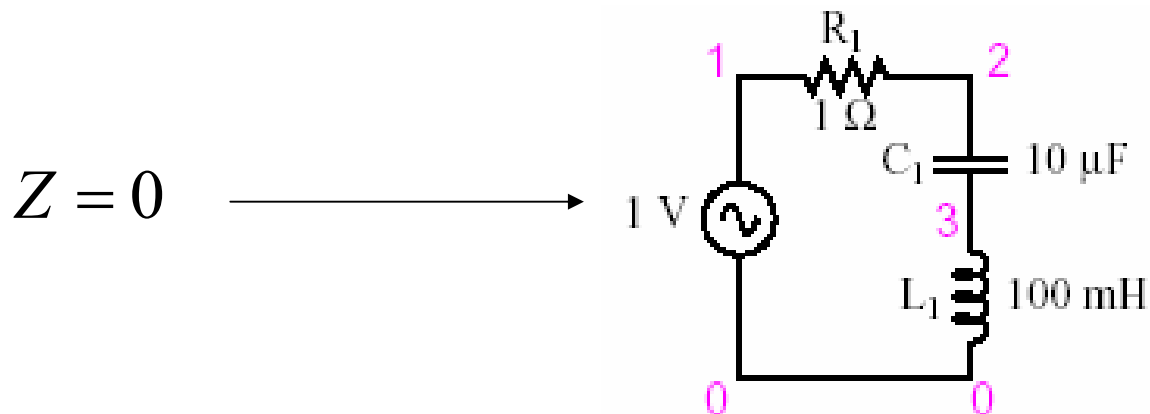- So the tank circuit behaves as an open circuit at resonance!
- In a very similar way one can show that a series LC circuit behaves as a short circuit when driven on resonance i.e.,



RLC series circuit

- 2nd order ODE:

$$RI + L \frac{dI}{dt} + \frac{Q}{C} = V$$


Voltage across capacitor

$$\text{with } I = \frac{dQ}{dt}; Q = CU$$

$$\Rightarrow LC \frac{d^2 U(t)}{dt^2} + RC \frac{dU(t)}{dt} + U(t) = V(t)$$

- Resonant frequency still $\omega_0 = \frac{1}{\sqrt{LC}}$
- Let's define the parameter $\zeta = \frac{R}{2L}$

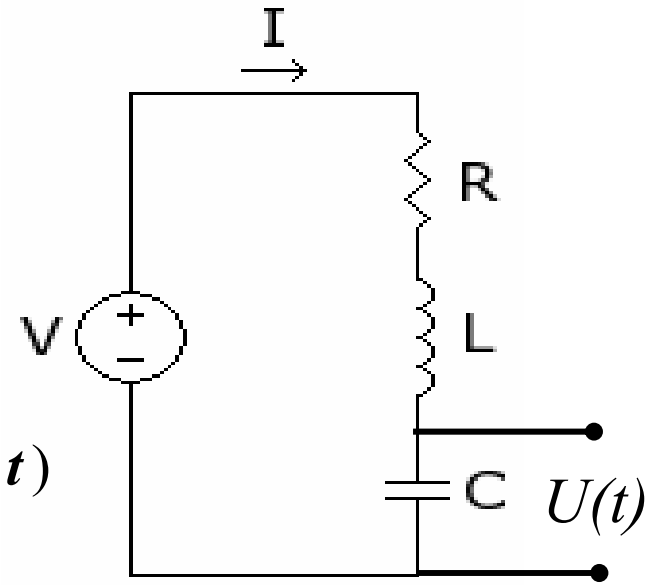- Then the ODE rewrites $\frac{d^2 U}{dt^2} + 2\zeta \frac{dU}{dt} + \omega_0^2 U = V$



RLC series circuit: regimes of operation (1)

- Let's consider $V(t)$ to be a dirac-like impulsion (not physical...) at $t=0$. Then for $t>0$, $V(t)=0$ and the previous equation simplifies to

$$\frac{d^2U}{dt^2} + 2\zeta \frac{dU}{dt} + \omega_0^2 U = 0$$

- With solutions

$$U(t) = Ae^{\lambda_+ t} + Be^{\lambda_- t}$$

- Where the λ are solutions of the characteristics polynomial is

$$\lambda^2 + 2\zeta\lambda + \omega_0^2 = 0$$

- The discriminant is

$$\Delta = R^2 C^2 - 4LC$$

- And the solutions are

$$\lambda_{\pm} = \frac{1}{2}(-2\zeta \pm \sqrt{\Delta})$$

RLC series circuit: regimes of operation (2)

- If $\Delta < 0$ that is if $R < 2\sqrt{\frac{L}{C}}$
Under damped

$$\lambda_{\pm} = -\frac{R}{2L} \pm \left[\left(\frac{R}{2L} \right)^2 - \frac{1}{LC} \right]^{1/2} \equiv -\delta \pm \sqrt{\delta^2 - \omega_0^2}$$

$U(t)$ is of the form

$$U(t) = e^{-\delta t} \left[A e^{\sqrt{\delta^2 - \omega_0^2} t} + B e^{-\sqrt{\delta^2 - \omega_0^2} t} \right]$$

A and B are found from initial conditions.

- If $\Delta = 0$ critical damping

$$U(t) = A e^{-\delta t}$$

RLC series circuit: regimes of operation (3)

- If $\Delta > 0$ that is if $R > 2\sqrt{\frac{L}{C}}$
Strong damping

$$\lambda_{\pm} = -\frac{R}{2L} \pm i \left[\frac{1}{LC} - \left(\frac{R}{2L} \right)^2 \right]^{1/2} \equiv -\delta \pm i \sqrt{\omega_0^2 - \delta^2}$$

$U(t)$ is of the form




$$U(t) = e^{-\delta t} \left[A e^{i \sqrt{\omega_0^2 - \delta^2} t} + B e^{-i \sqrt{\omega_0^2 - \delta^2} t} \right]$$

A and B are found from initial conditions.

Which can be rewritten

$$U(t) = D e^{-\delta t} \sin \left(\sqrt{\omega_0^2 - \delta^2} t + \phi \right)$$

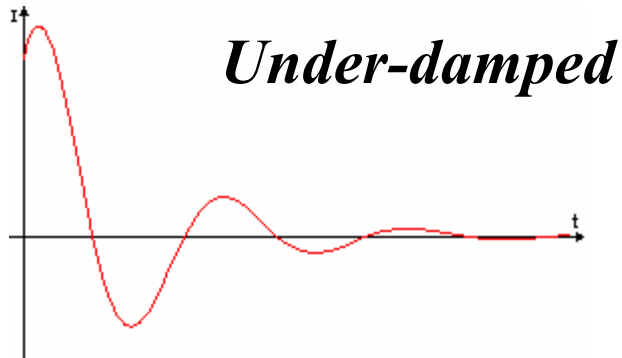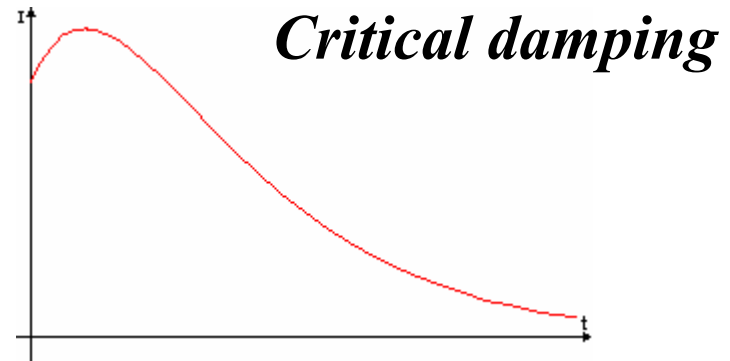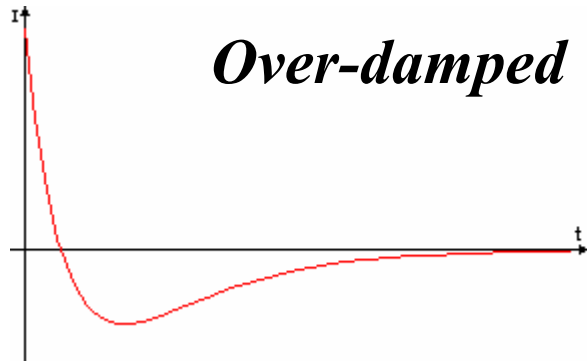RLC series circuit: regimes of operation (4)




- For **under-damped regime**, the solutions are exponentially decaying sinusoidal signals. The time required for these oscillations to die out is $1/Q$ where the quality factor is defined as:

$$Q \equiv \frac{1}{R} \sqrt{\frac{L}{C}}$$

RLC series circuit: Impedance (1)

- 2nd order ODE:
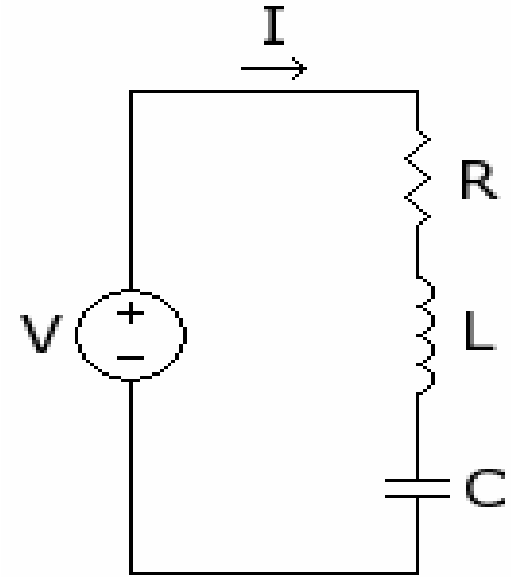
$$V = V_R + V_L + V_C = RI + L \frac{dI}{dt} + \frac{1}{C} \int I dt$$
$$\Rightarrow \frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = \frac{1}{L} \frac{dV}{dt}$$



- Resonant frequency still $\omega_0 = \frac{1}{\sqrt{LC}}$
- Let's define the parameter $\zeta = \frac{R}{2L}$
- Then the ODE rewrites

$$\frac{d^2 I}{dt^2} + 2\zeta \frac{dI}{dt} + \omega_0^2 I = \frac{1}{L} \frac{dV}{dt}$$

RLC series circuit: Impedance (2)

- Take back (but could also just compute the impedance of the system)

$$\frac{d^2 I}{dt^2} + 2\zeta \frac{dI}{dt} + \omega_0^2 I = \frac{1}{L} \frac{dV}{dt}$$

- Explicit I in its complex form and deduce the current:


$$-\omega^2 I + 2i\zeta\omega I + \omega_0^2 I = i \frac{1}{L} \omega V$$

$$\Rightarrow Y \equiv \frac{I}{V} = \frac{i\omega}{\omega_0^2 - \omega^2 + 2i\zeta\omega} \Rightarrow |Y| = \frac{1}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

- Introducing $x = \omega/\omega_0$ we have

$$|Y| = \frac{1}{R \sqrt{1 + Q^2 \left(x - \frac{1}{x}\right)^2}}$$

RLC series circuit: resonance

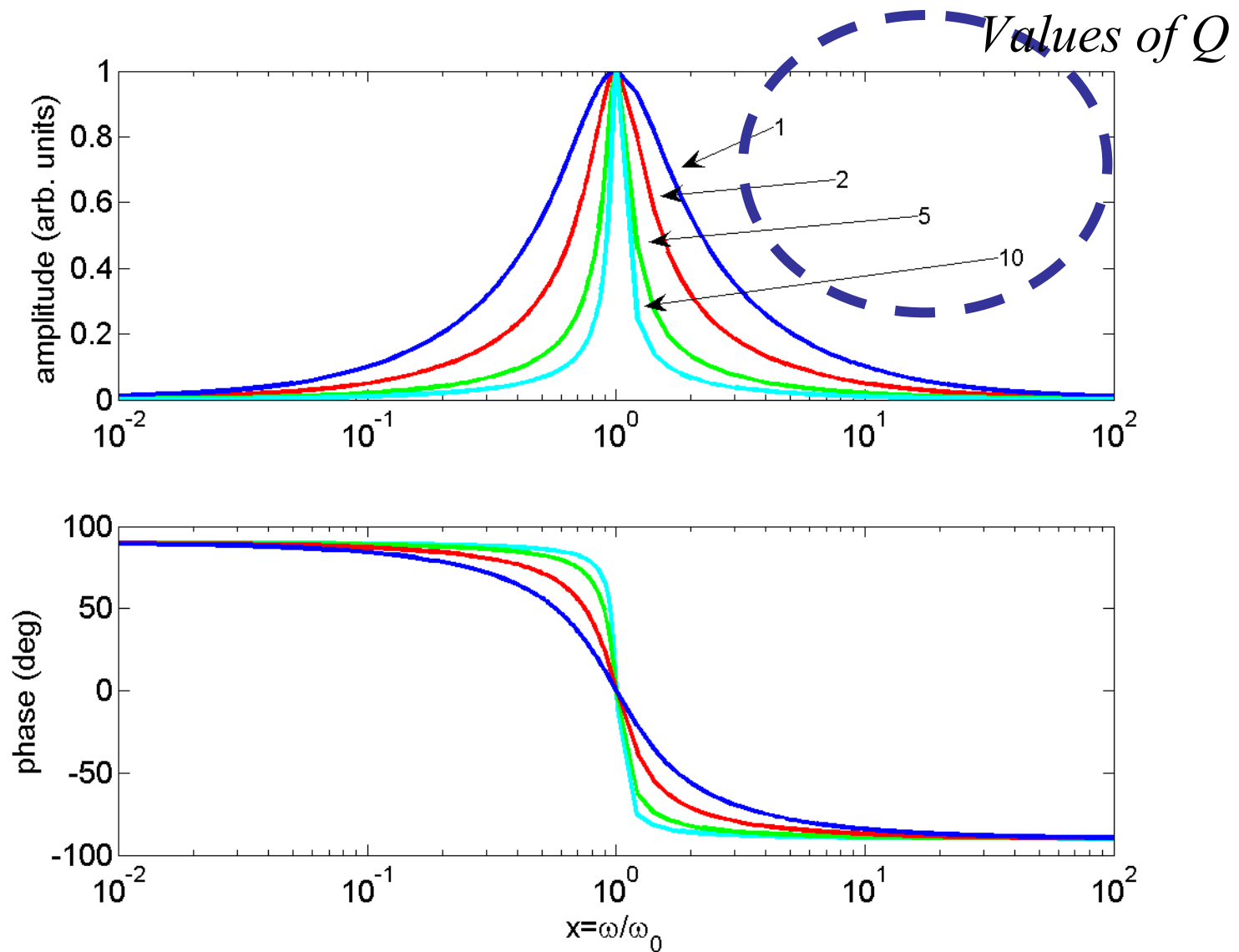

RLC parallel circuit : resonance

- The same formalism as before can be applied to parallel RLC circuits.
- The difference with serial circuit is: at resonance the impedance has a maximum (and not the admittance as in a serial circuit)