

# Lesson 4: Signal transmission & Noise

---

- **Signal Transmission**
  - Coupling scheme
  - Transmission line
  - Termination & impedance matching
- **Noise**
  - White noise
  - Pink noise
  - Lock-in amplifier: measuring modulated signal buried into noise




# Signal transmission

---

- There is often a need to propagate a signal over long distance
- This is accomplished with a transmission line in electronics
- Fancier system convert electronic signal into an optical pulses and use fiber to propagate signal over very long distance (e.g. communication cable under Atlantic ocean)
- The fundamental questions are:
  - How do we “inject” a signal into a transmission line
  - How do we model the effect of long transmission line on the electrical signal
  - How do we “terminate” the transmission line to get an handle on the signal and avoid reflections and/or interferences
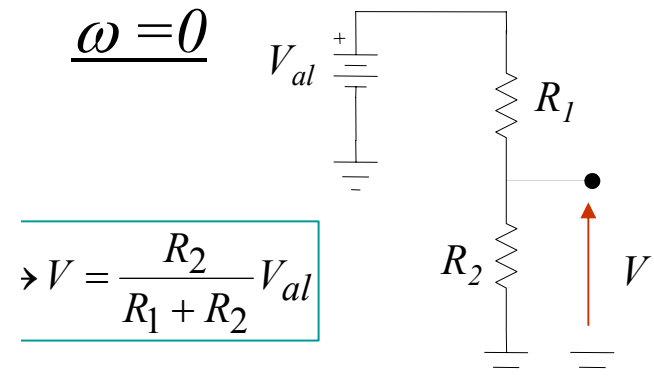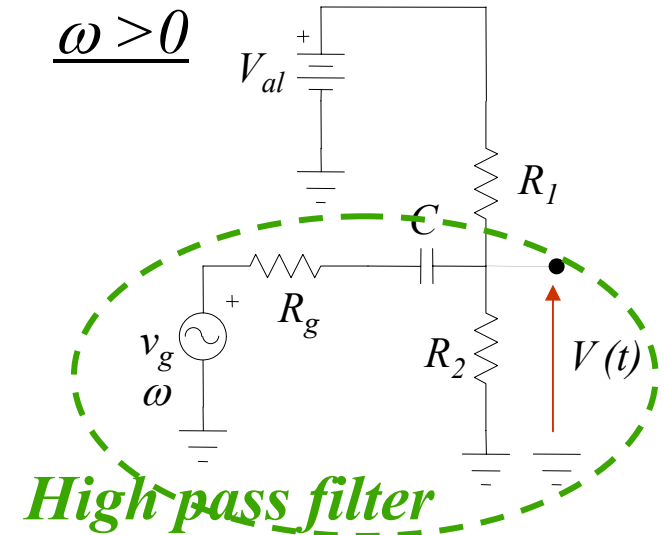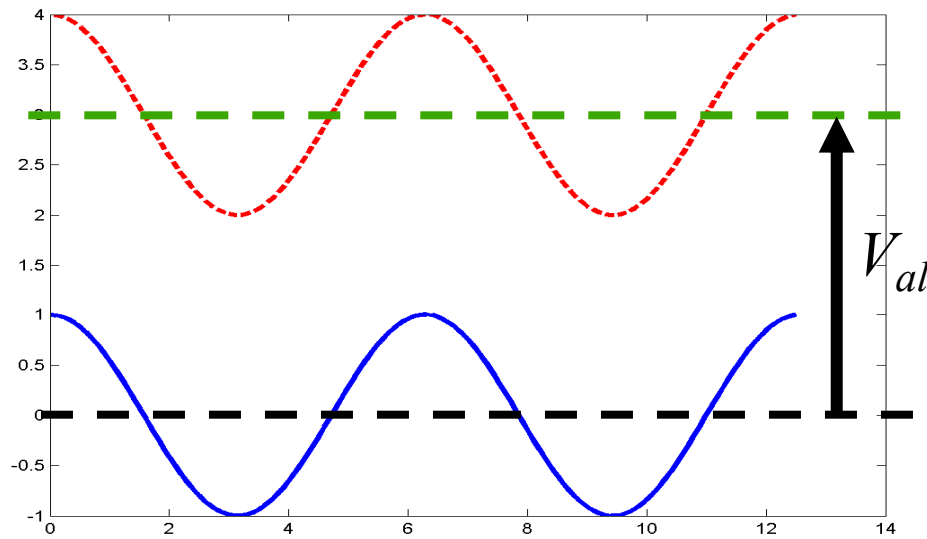
# Capacitive Coupling


- A simple RC filter is used to block DC component
- An DC voltage source offset the average of  $V(t)$ .



# Inductive Coupling: transformer

- Transformer can be used as “couple

Transformer

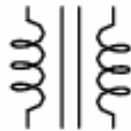


- Transformer equation

$$\left. \begin{aligned} v_P &= N_P \frac{d\Phi}{dt} \\ v_S &= N_S \frac{d\Phi}{dt} \end{aligned} \right\} \frac{v_P}{v_S} = \frac{N_P}{N_S} \quad \frac{i_P}{i_S} = \frac{N_S}{N_P}$$

- Output impedance of the system:

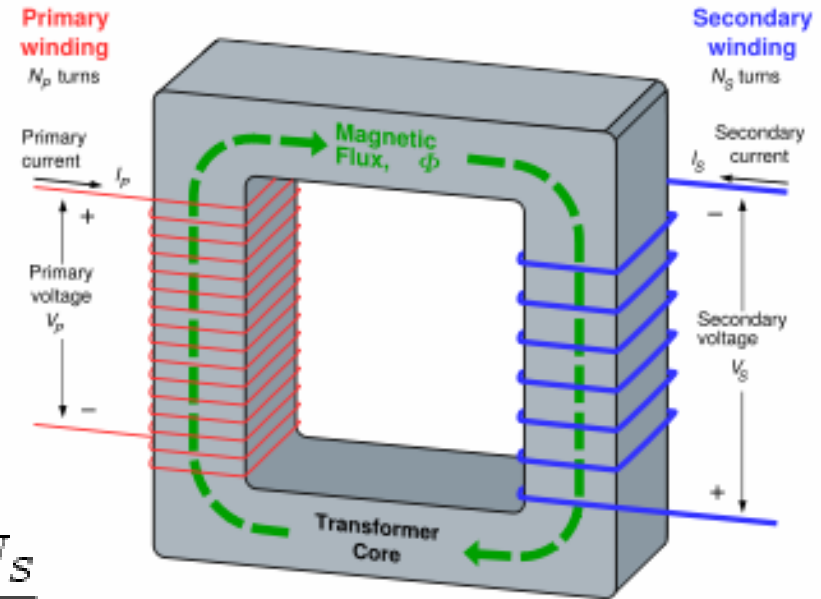
$$Z_{\text{output}} = n^2 Z_{\text{input}}, \quad n \equiv \frac{N_P}{N_S}$$


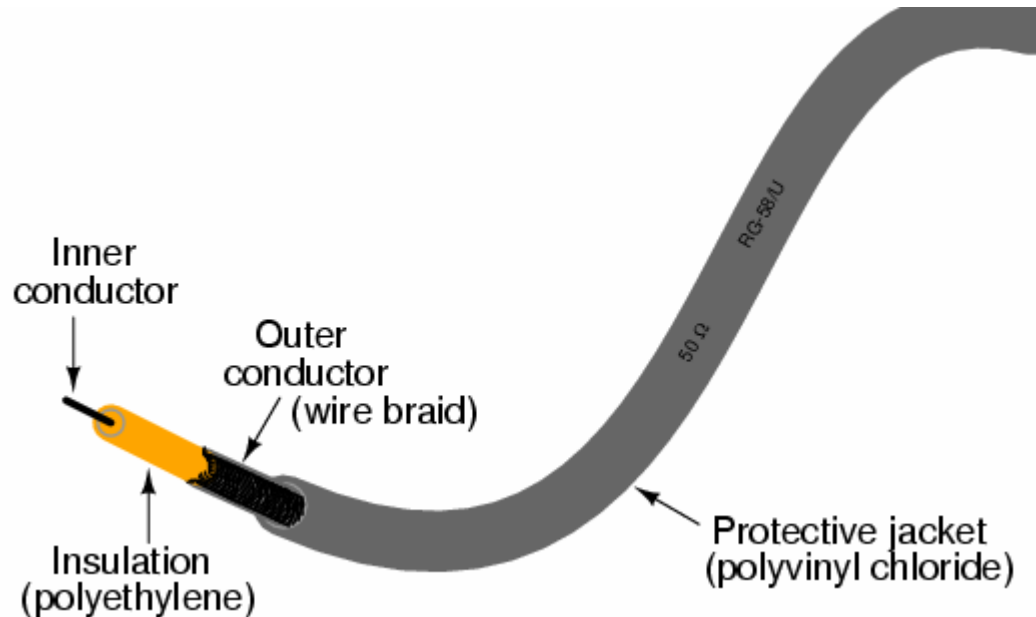
# Transmission line: coaxial cable

---


- You already used this cable in the Lab (to connect oscilloscope or frequency generator to your circuits)



- How do we model this cable?

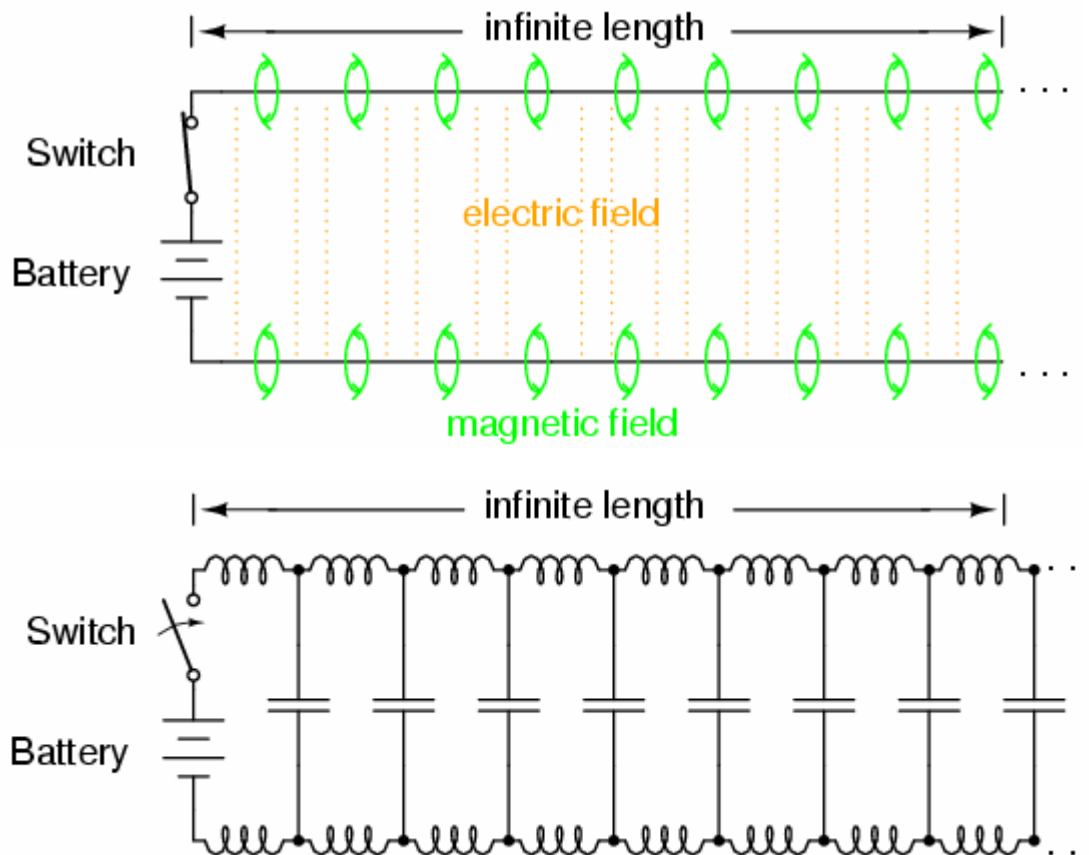
# Transmission line: coaxial cable

- Coaxial cable can be model as a chain of inductance and capacitance (there is also some resistance of course)


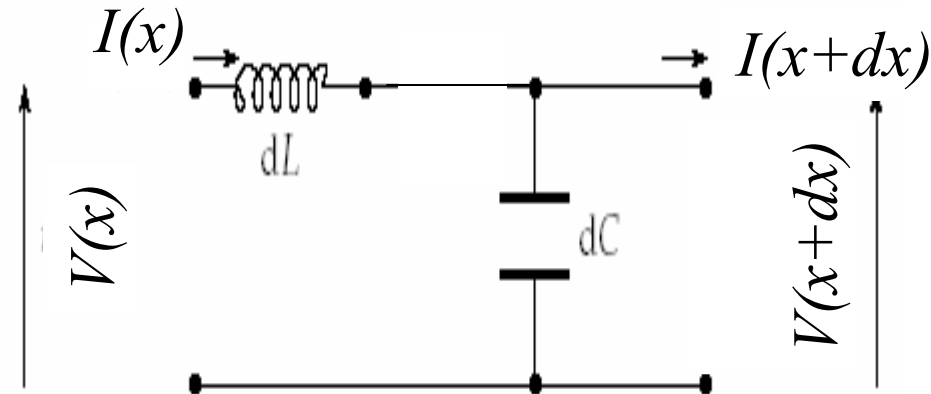
# Transmission line: “Wave equation”

- Introduce the capacitance  $dC=c_0dx$  and inductance  $dL=l_0dx$  per unit of length.
- We can apply Kirchhoff's voltage and current law to an LC cell of the circuit



$$\begin{cases} I(x) = I(x+dx) + c_0 \frac{dV(x)}{dt} \\ V(x) = V(x+dx) + l_0 \frac{dI(x+dx)}{dt} \end{cases}$$

$$\frac{dI}{dx} = -c_0 \frac{dV}{dt}$$

$$\frac{dV}{dx} = -l_0 \frac{dI}{dt}$$

$$\frac{d^2V}{dx^2} - l_0 c_0 \frac{d^2V}{dt^2} = 0$$

*wave equation*

# Solution of wave equation

---

- So the wave equation is satisfied by both  $I$  and  $V$

$$\frac{d^2}{dx^2} \begin{pmatrix} V \\ I \end{pmatrix} - l_0 c_0 \frac{d^2}{dt^2} \begin{pmatrix} V \\ I \end{pmatrix} = 0$$

- This are wave equations (in electromagnetism both scalar and vector potentials associated to an e.m. wave obey this equation)

- The  $l_0 c_0$  quantity has the dimension  $[L^{-2}.T^2]$ :  $v \equiv \frac{1}{\sqrt{l_0 c_0}}$
- The solution of the wave equation are of the form:

$$I(x, t) = I_0 e^{i(\omega t - kx)} + I_1 e^{i(\omega t + kx)}$$

$$V(x, t) = Z[I_0 e^{i(\omega t - kx)} - I_1 e^{i(\omega t + kx)}]$$

*Forward TW*


*Backward TW*



# Coaxial cable impedance

- Plugging traveling wave solution into 1<sup>st</sup> differential equation directly gives a relation between  $V$  and  $I$

$$Z \equiv \sqrt{\frac{l_0}{c_0}}$$

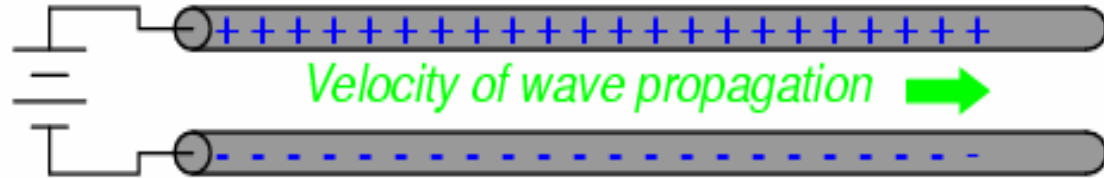

- A cable can be treated as an element with the above impedance.

$$\text{Velocity factor} = \frac{v}{c} = \frac{1}{\sqrt{\epsilon_r}}$$

Where,

- Impedance of the cable is independent of its length!**
- signal propagates with velocity close to  $c$  (actually  $c/n$ )**

$v$  = Velocity of wave propagation

$c$  = Velocity of light in a vacuum

$\epsilon_r$  = Relative permittivity of insulation between conductors

# Termination: Impedance matching

---

- Suppose at  $x=L$  we connect a resistor with resistance  $R$  then, at  $x=L$  we have

$$V(x=L, t) = RI(x=L, t)$$

$$\Rightarrow Z[I_0 e^{i(\omega t - kL)} - I_1 e^{i(\omega t + kL)}] = R[I_0 e^{i(\omega t - kL)} + I_1 e^{i(\omega t + kL)}]$$

$$\Rightarrow I_1 = \frac{R - Z}{R + Z} I_0 e^{-2ikL}$$

- So the current and voltage take the form

$$I(x, t) = I_0 [e^{i(\omega t - kx)} - r e^{i(\omega t + kx)}]$$

$$V(x, t) = Z I_0 [e^{i(\omega t - kx)} + r e^{i(\omega t + kx)}]$$

with  $r$  being a reflection coefficient  $r \equiv \frac{I_1}{I_0}$

- $r=0$  if  $Z=R$  (impedance matching)
- Situation more complicated in practice since signal not really monochromatic**

# Termination: Impedance matching

---

- If **termination is open** ( $R \rightarrow \infty$ ) then  $r = \exp(-i2kL)$  and the voltage becomes

$$V(x, t) = 2V_0 \cos(\omega t - kL) \cos k(x - L)$$


this is a stationary wave!

- If **termination is closed** (*short circuit*:  $R=0$ ) then  $r = -\exp(-i2kL)$  and the voltage becomes


$$V(x, t) = -2V_0 \sin(\omega t - kL) \sin k(x - L)$$

this is again a stationary wave!

# Termination: case of open end

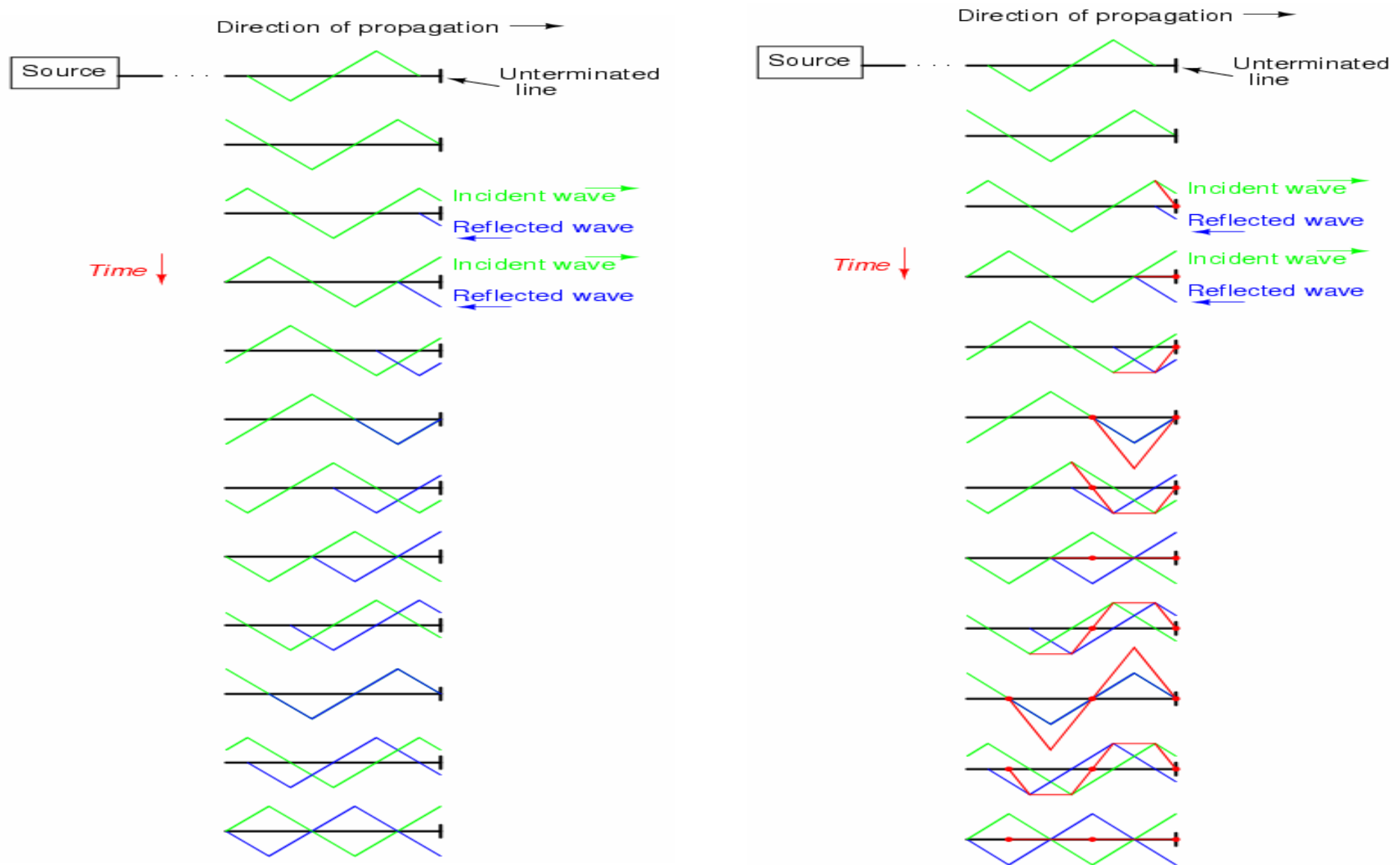

# Termination: case of open end (CNT'D)

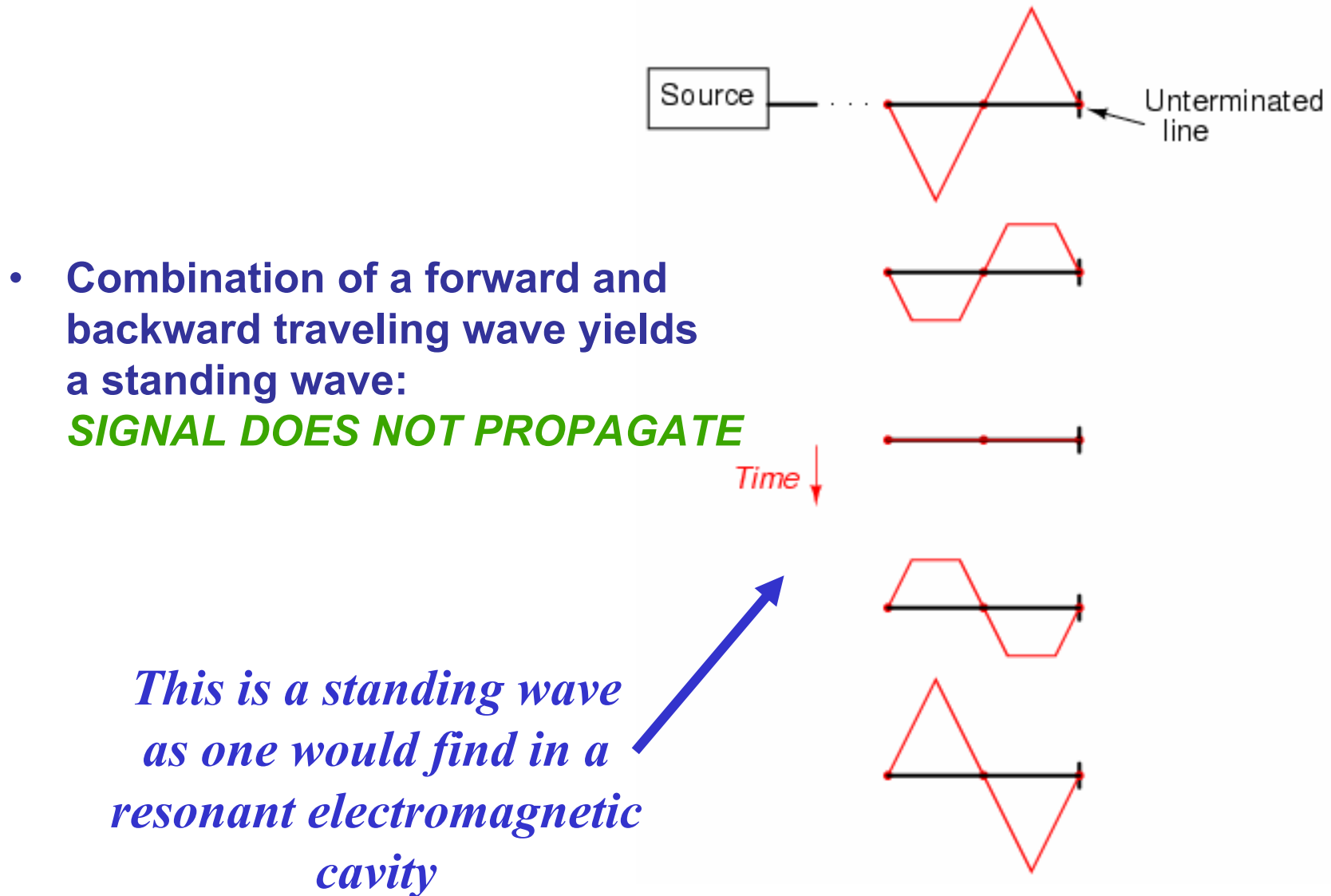

# Noise: Thermal Noise (or Johnson–Nyquist noise )

---

- In a conductor electron have random motion due to temperature.
- The **power spectral density** (= mean square voltage per unit of frequency in **V<sup>2</sup>/Hz**) associated to this thermal noise is:

$$\frac{d\langle V^2 \rangle}{df} = 4kTR \frac{hf}{kT} \frac{1}{e^{\frac{hf}{kT}} - 1} \approx 4kTR$$

*“Low” frequency ( $f < 1$  GHz) approximation*

*R: resistance,  
k: Boltzmann const.  
h: Planck const.  
T: temperature [K]  
f: frequency [Hz]*

- So the rms voltage noise is  $\langle V^2 \rangle^{1/2} = 2\sqrt{kTR\Delta f}$

*Frequency bandwidth*

- and the rms current noise is  $\langle I^2 \rangle^{1/2} = 2\sqrt{\frac{kT\Delta f}{R}}$

# Noise: Shot Noise

---

- Shot noise comes from the fact that current is generated by a FINITE amount of discrete charge carried by electrons
- The current fluctuate with a probability following Poisson's distribution with variance

$$\langle I^2 \rangle^{1/2} = \sqrt{2 |e| \langle I \rangle \Delta f}$$

*e: electron charge*

*$\Delta f$ : frequency bandwidth [Hz]*

- Through a resistor this introduces a power fluctuation

$$\langle P^2 \rangle^{1/2} = 2R |e| \langle I \rangle \Delta f$$

# Noise: Flicker Noise (1/f )

- Shot and Thermal noise are white noise (no frequency dependence on power)


- Colored noise also exist typically

$$\frac{d\langle V^2 \rangle}{df} \propto \frac{1}{f^\alpha}$$

- When  $\alpha=1$  noise is referred to as “**pink**” noise or **1/f** noise

- In electronics pink noise is due to a variety of cause: impurity, carrier/hole recombination, ...

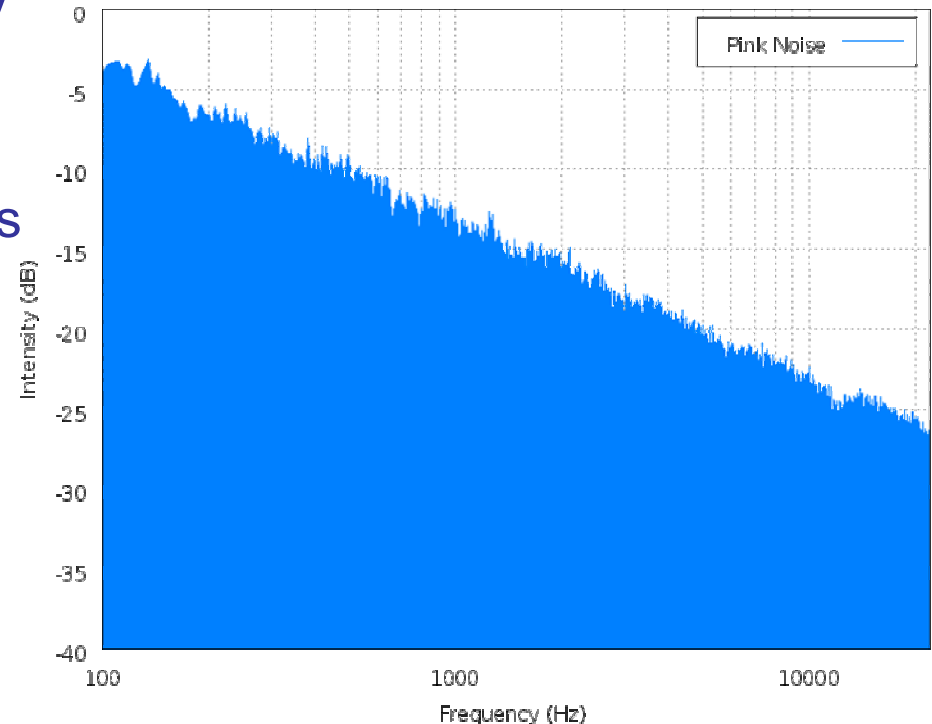- Flicker noise appear for instance in resistors and transistors





# How do we deal with and characterize noise?

---

- Work with small bandwidth system, optimize the bandwidth for the signal
- Can use RC filter to cut both hand of the spectrum
- A figure-of-merit to quantify noise compared to the main signal is the S/N ratio  $(S / N)_{Db} \equiv 10 \log_{10} \left( \frac{S}{N} \right)$
- Most of the time engineers like to express this S/N ratio as the unit of S/N is this latter expression is **Decibel** (Symbol Db)
- Some practical “conversion”:  $S / N \equiv \frac{P_{signal}}{P_{noise}}$   
 $S / N = 10 \Leftrightarrow (S / N)_{Db} = 10 \text{ Db}$   
 $S / N = 2 \Leftrightarrow (S / N)_{Db} \approx 3 \text{ Db}$   
 $S / N = 1 / 2 = 0.5 \Leftrightarrow (S / N)_{Db} \approx -3 \text{ Db}$

# How do we deal with and characterize noise?

---

- The effect of a system on the noise is quantified by a noise factor:

$$F = 10 \log_{10} \frac{(S / N)_{OUT}}{(S / N)_{IN}}$$

- Design system such that  $F < 1$  (to reduce noise)
- Sometime one has to “live” with noise and use some experimental technique to recover the signal buried in the noise; very typical in low light detection experiments for instance...


This is accomplished by using a so-called Lock-in amplifier

# Detection of ultra-low signal buried in noise: The lock-in amplifier

---

$$A = A \cos(\omega t) + N$$


$$B = B \cos(\omega t + \varphi)$$

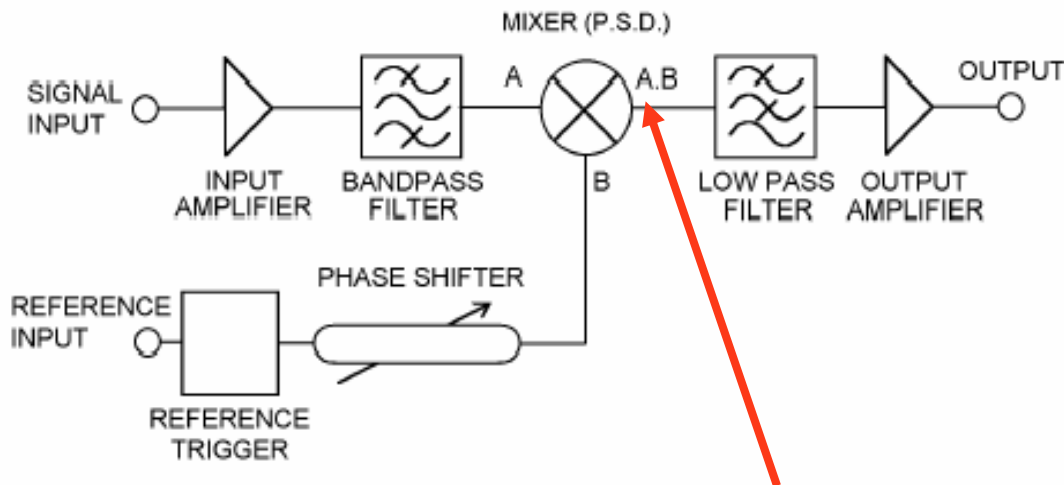


$$\begin{aligned} AB &= \hat{A}\hat{B} \cos(\omega t) \cos(\omega t + \varphi) + \hat{A}N \cos(\omega t + \varphi) \\ &= \frac{\hat{A}\hat{B}}{2} [\cos(2\omega t + \varphi) + \cos(\varphi)] + \hat{A}N \cos(\omega t + \varphi) \end{aligned}$$

*What remains after  
low pass filter*


# Lock-in amplifier: a numerical example

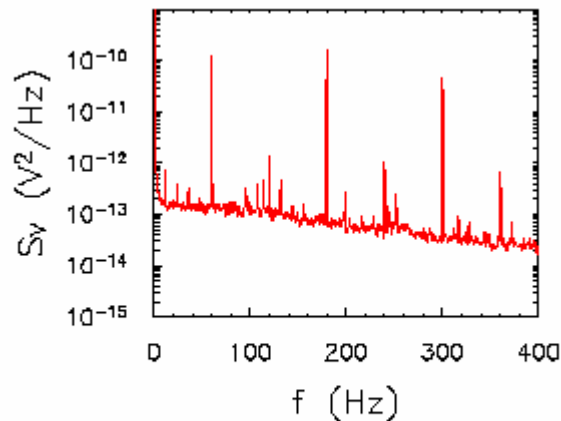


**Figure 3.** Graph of the power spectral density of the input signal. The desired signal is the "spike" at 200 Hz. Other spikes are due to unwanted pickup from the 110 VAC line at 60 Hz and its harmonics.

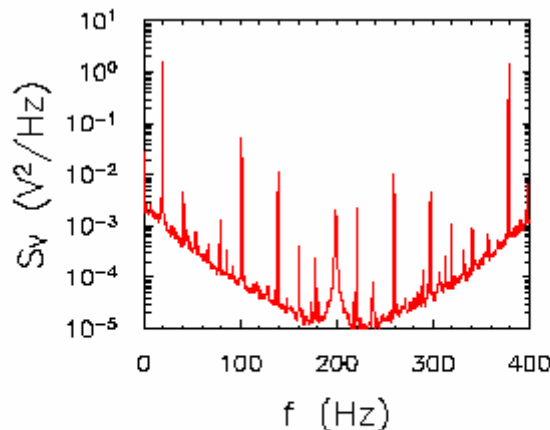

**Figure 5.** Power spectral density of the output of the multiplier stage. The effect of beating has shifted each spike at frequency  $f$  in Figure 4 to two new positions,  $200 \text{ Hz} + f_i$  and  $200 \text{ Hz} - f_i$ . The desired signal is now located at zero frequency and at 400 Hz. The broad spike now located at 200 Hz is mostly associated with the  $1/f$

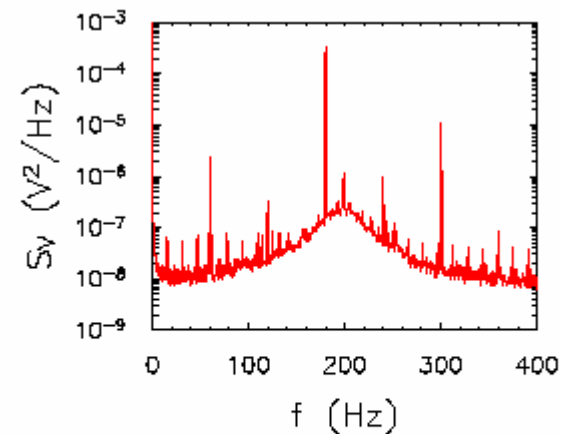

**Figure 4.** Power spectral density of the output of the AC amplifier stage. The bandpass character allows the desired frequency of 200 Hz to be amplified while frequencies well away from 200 Hz are attenuated. In particular we have reduced the effects of line frequency pickup and the  $1/f$  noise near DC.

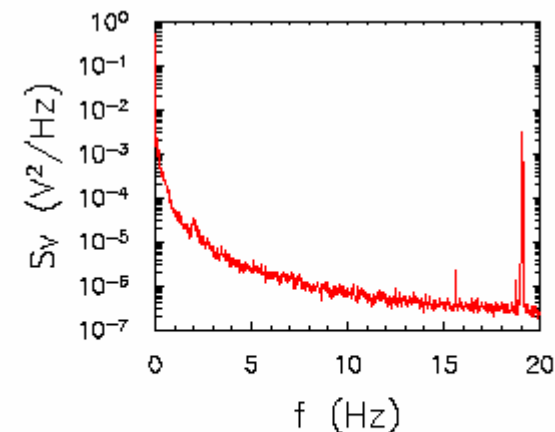

**Figure 6.** Power spectral density at the output of the DC amplifier. Note the change in frequency scale from the earlier plots. The desired signal at DC is now the only significant signal since the low-pass filter has removed everything above 1 Hz. Though difficult to see on the graph,  $S_V(0) = 0.55 \text{ V}^2/\text{Hz}$ .