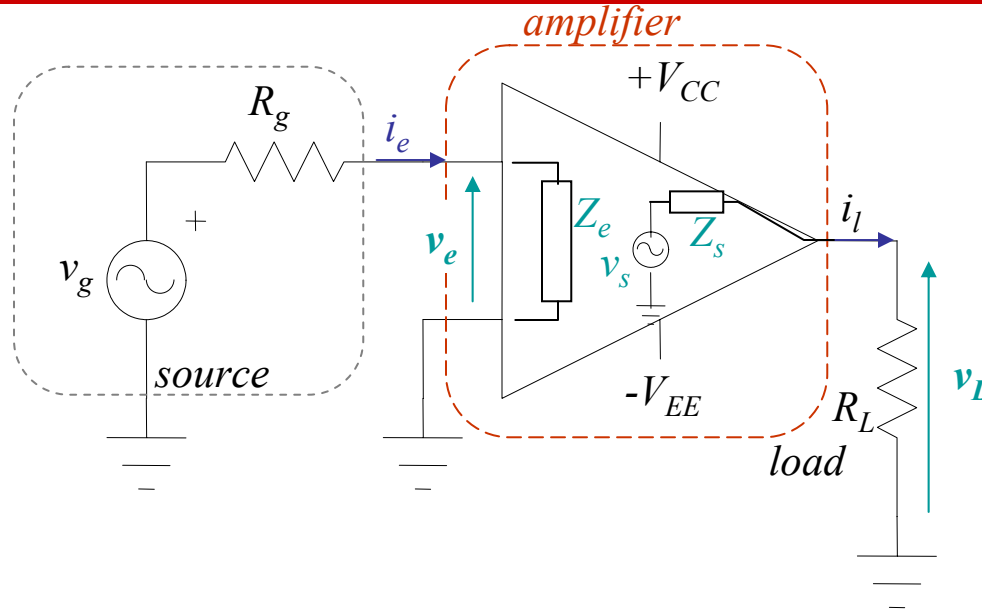


Amplifier and feedback systems

- **Amplifier system**
- **Feedback system**

Amplifier



- **Function:** amplify the “signal” power
 → amplifiers are powered by an external source [here: V_{CC} **and (or)** V_{EE}]
- **Input** of amplifier characterized by the **input impedance** $Z_e = \frac{v_e}{i_e}$
- The amplifier **output** acts as a voltage **source** characterized by its **output impedance** Z_s
 ! Z_s = **Thévenin** equivalent resistance of the circuit “seen” by R_L

Gain(s) definition

● Voltage gain:

Since $\mathbf{Z_s \neq 0}$, voltage gain **depends** on load

Gain “in open circuit” :

$$A_v = \left. \frac{v_L}{v_e} \right|_{R_L = \infty} = \frac{v_s}{v_e}$$


Gain “on load” :

$$A_{vL} = \frac{v_L}{v_e} = \frac{R_L}{R_L + Z_s} A_v$$

“composite” gain:
(take into account
the output impedance)

$$A_{vc} = \frac{v_L}{v_g} = \frac{Z_e}{R_i + Z_e} A_{vL}$$

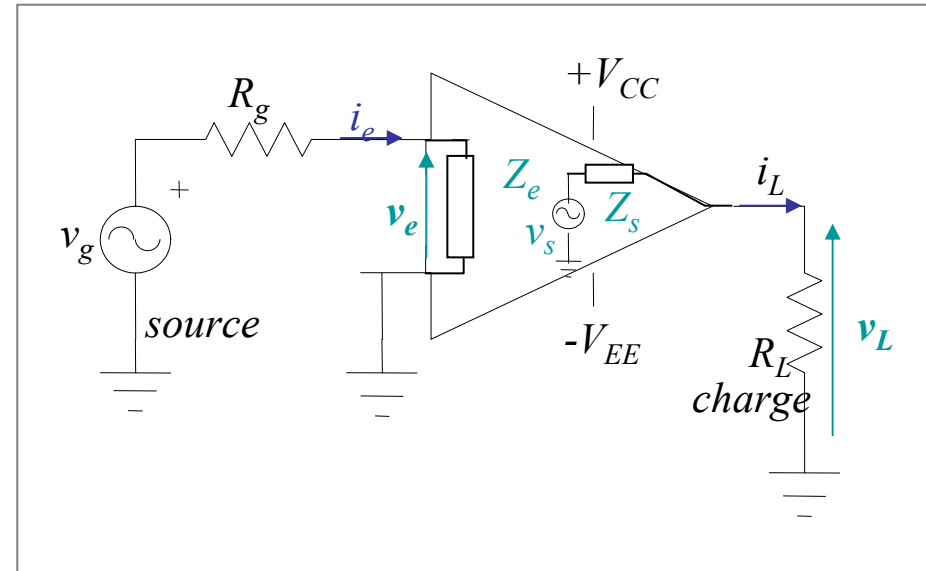Since $\mathbf{Z_e \neq \infty}$, A_{vc} different from A_{vL}



● Current gain

$$A_i = \frac{i_L}{i_e} = \frac{A_{vL} Z_e}{R_L}$$

● Power gain :

$$A_p = \frac{v_L i_L}{v_g i_e} = A_{vc} \cdot A_i$$

Ideal amplifier

- Gains independent of amplitude and frequency of input signal
- Entrance impedance high \Leftrightarrow **low perturbation on the source operation**
- Exit impedance low \Leftrightarrow **small perturbation of the load**


Real life...

- **linearity regime : distortion** of signal occurs for high amplitudes
Nonlinearities of some electronics characteristics
- **limited frequency bandwidth** : gain is a function of signal frequency
 - internal capacitance of some components
 - capacitors used in the circuits
 - input and output impedances depend on frequency

Feedback Systems


- **Closed loop:**

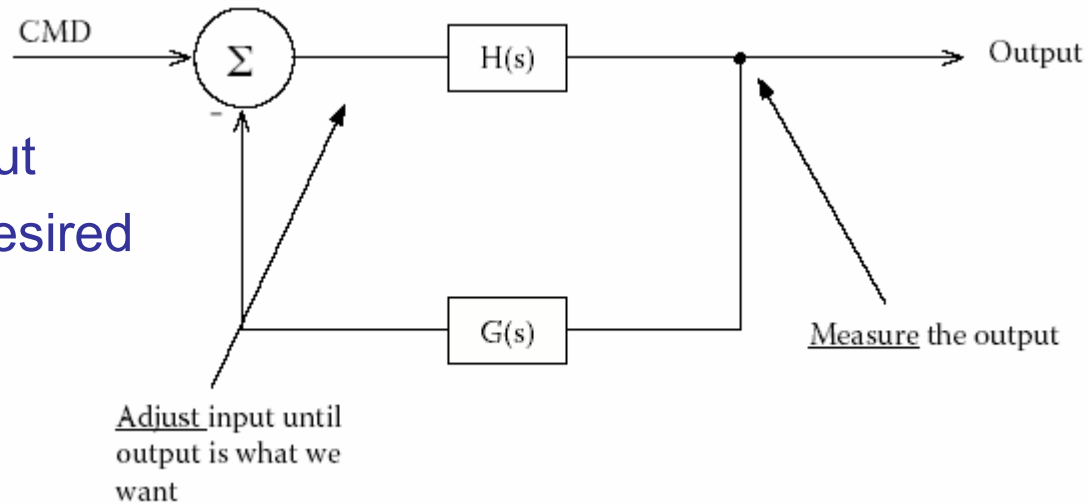- Measure output
- Compare to desired output signal
- Correct input accordingly



- **Open loop**

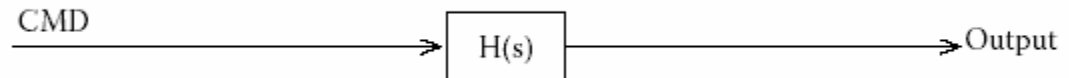- Design or characterize the transfer function of the system
- Apply a proper input so that output signal is the desired value



Feedback Systems (real life... almost)

- Open loop


- Adjust flow and on/off until water reach expected value
- Your eyes are closed

Fill glass to here exactly




- Closed loop

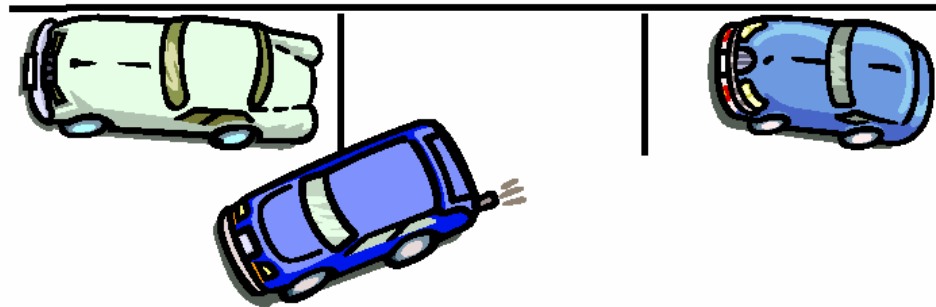- Set of constraints
- Measurement (trust your vision)



Voltage feedback

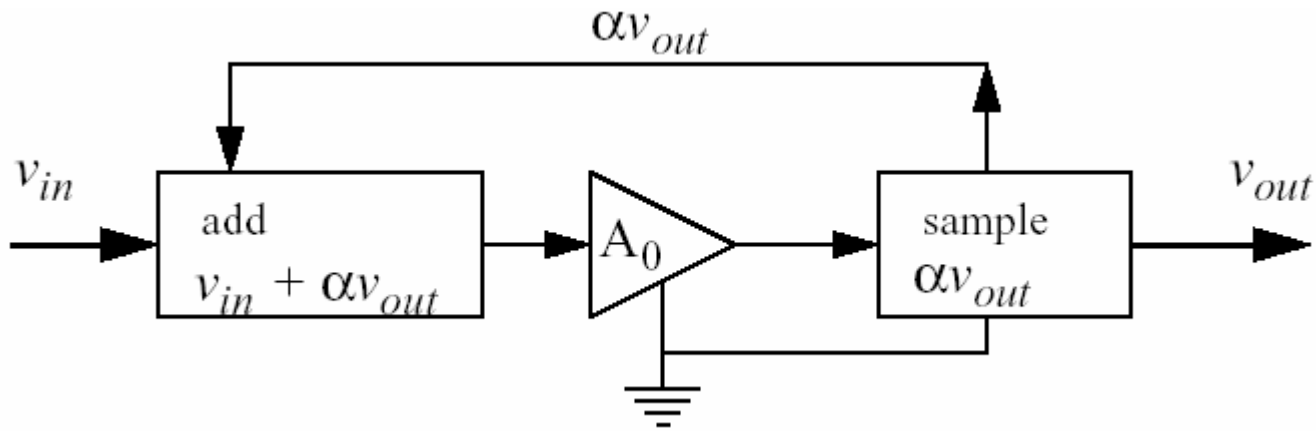- Sample part of the output voltage and feedback as input



- Gain of the system is (assume $A_0 \gg 1$)

$$A = \frac{v_{out}}{v_{in}} = \frac{A_0}{(1 - A_0 \alpha)}$$

problem is $A_0 \alpha$ close to 1

Voltage feedback

- Gain stability

$$\frac{dA}{A} = \frac{dA_0}{A_0} - \alpha \frac{dA_0}{(1 - A_0 \alpha)} = \frac{A}{A_0} \frac{dA_0}{A_0}$$

- Small change in A_0 gain results in change in A

- Input impedance changes


$$Z_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in0}}{(1 + \alpha A) i_{in}} = \frac{A_0}{A} Z_{in0}$$

- Output impedance also changes

$$Z_{out} = \frac{v_{out}}{i_s} = \frac{A v_{in}}{i_s} = \frac{A i_s Z_{out0}}{i_s A_0} = \frac{A}{A_0} Z_{out0}$$

Current feedback

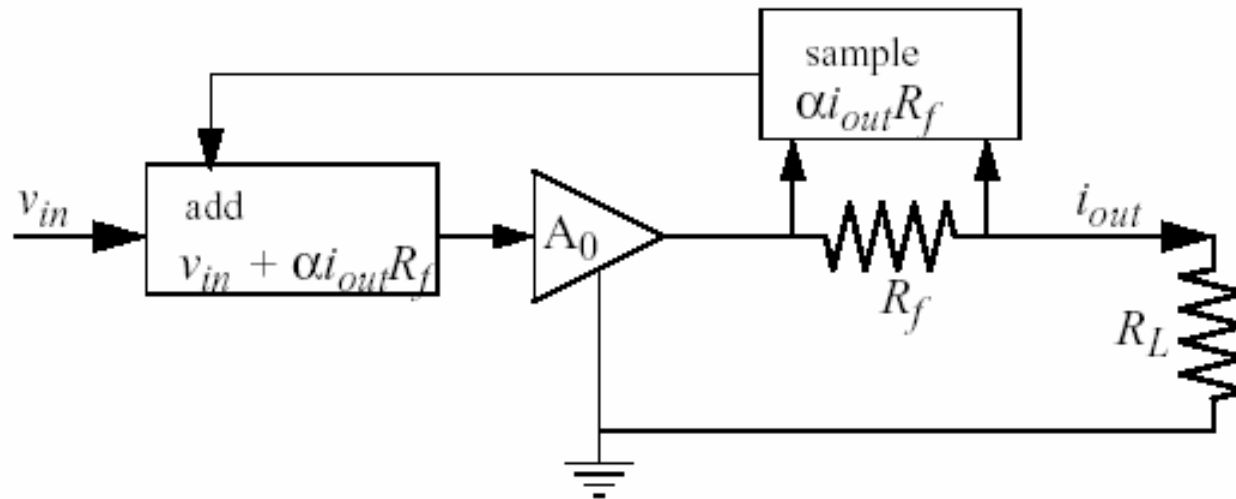- Sample output current, convert to voltage and add to input



$$i_{out} = \frac{A_0 v_{in}}{R_L + Z_{out0} + (1 - A_0 \alpha) R_f}$$